

## ECE 304 Fall '04 Lab 1

### Objective

The behavior of a current mirror is simulated.

### Schematic

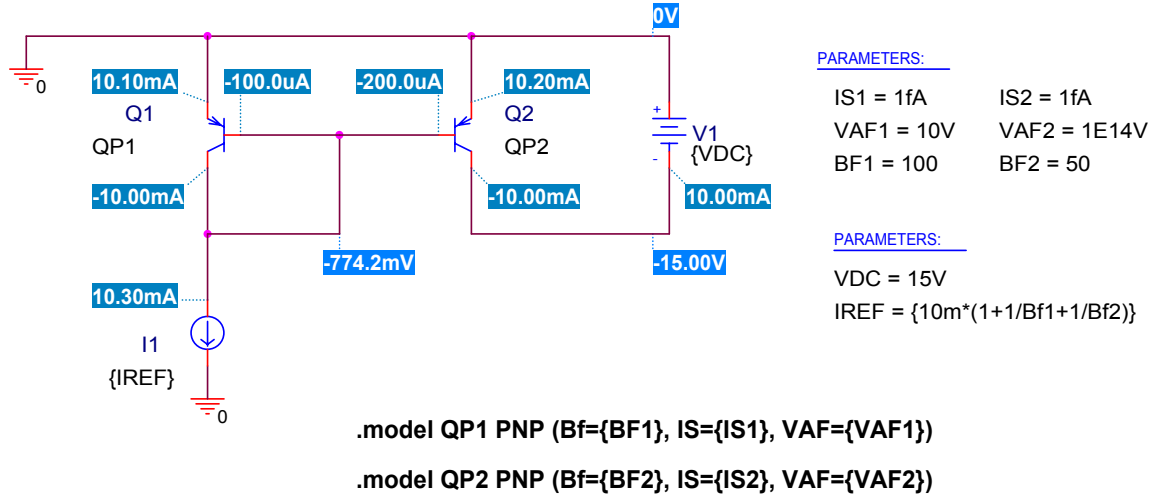


FIGURE 1

Schematic for current mirror; dot-model statements for the two devices are shown

### Discussion of non-ideal mirror behavior

Ideally, the current at the mirror output is the same as the current  $I_{REF}$ . However, this ideal behavior is seldom observed for the following reasons:

1. Transistors draw base current

The schematic in Figure 1 shows a current mirror for which the current  $I_{REF}$  is bigger than the output current by the contribution of the two base current for Q1 and Q2. The situation can be even less ideal if the scale current  $I_S$  of the two transistors are different, as shown in Figure 2.

2. Transistors have different scale currents  $I_S$ .

In Figure 2 it is seen that the output current is only half the reference current because of *mismatch* of the scale currents. That is,  $I_{S1} = 2fA$  and  $I_{S2} = 1 fA$ .


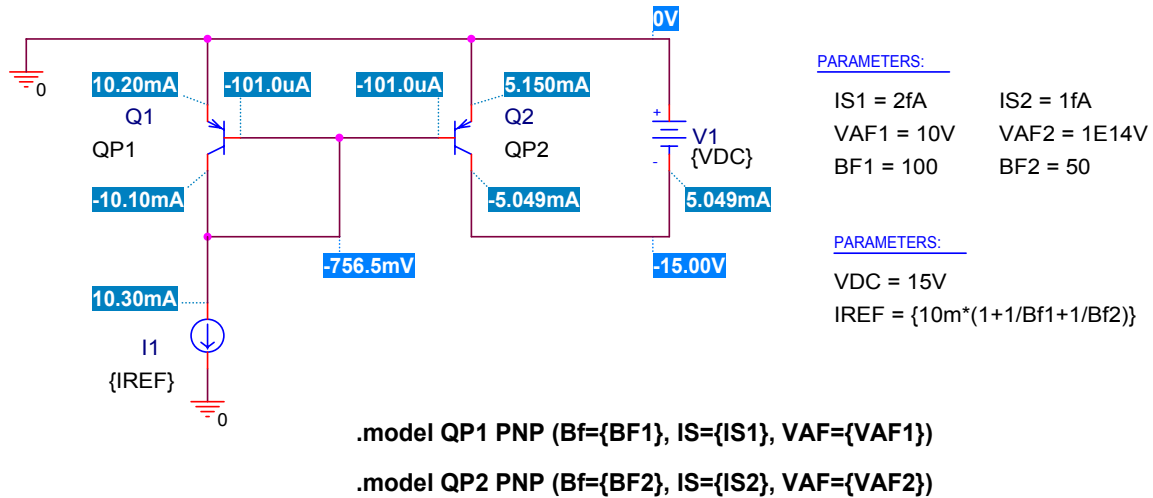


FIGURE 2

Same circuit as Figure 1 but transistors have different scale currents:  $I_{S1} = 2fA$ ,  $I_{S2} = 1 fA$ .

### 3. Early voltage and the Early effect

Another cause of non-ideal behavior is the Early voltage. In both Figure 1 and Figure 2 the Early voltage of Q2 is very large ( $V_{AF} = 1E14V$ ). This means that the output current of Q2 is nearly independent of the collector-base voltage  $V_{CB}$ . On the other hand, the current in Q1 is for  $V_{CB} = 0V$ , so its Early voltage does not matter. In Figure 3, both transistors are identical, but Q2 has  $V_{BC} = (-774mV + 15V) \approx 14.2V$ , while Q1 has  $V_{BC} = 0V$ . Because of the Early effect, the output current is much larger than  $I_{REF}$ .

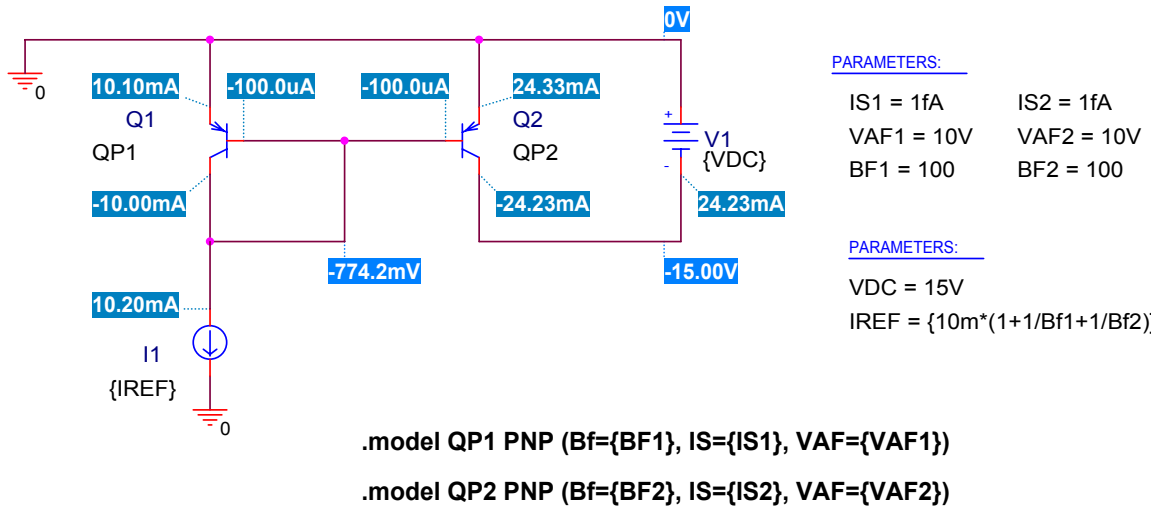

**FIGURE 3**  
Matched transistors, but different values of  $V_{CB}$


### Exercise

Taking the  $I$ - $V$  characteristic of the bipolar as  
**EQ. 1**

$$I_C = I_S e^{V_{EB}/V_T} \left( 1 + \frac{V_{BC}}{V_{AF}} \right),$$

where  $V_T$  = thermal voltage (about 25.864 mV at 27°C) analyze the circuit of Figure 1 to find the current in terms of  $I_{REF}$ ,  $I_{S1}$ ,  $I_{S2}$  and  $V_{AF1}$ ,  $V_{AF2}$ . Construct a spreadsheet to test your result. The spreadsheet should have the structure shown in Figure 4 with the CHARTS input page shown in Figure 5.

### Current Mirror

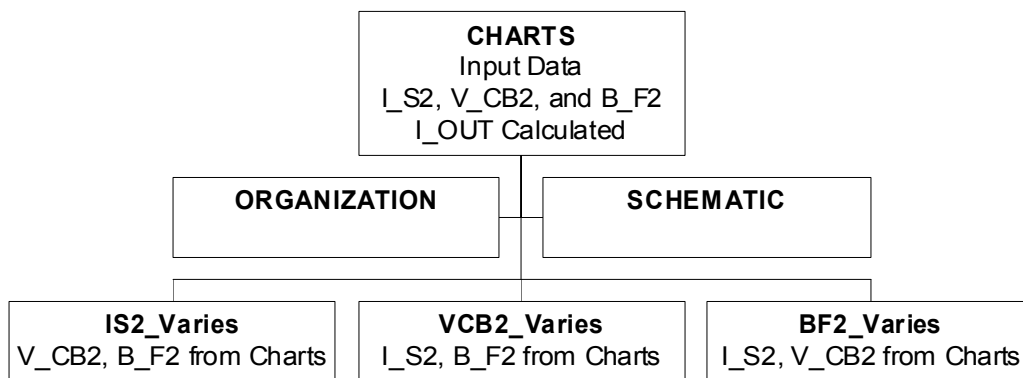

**FIGURE 4**  
Organization of spreadsheet

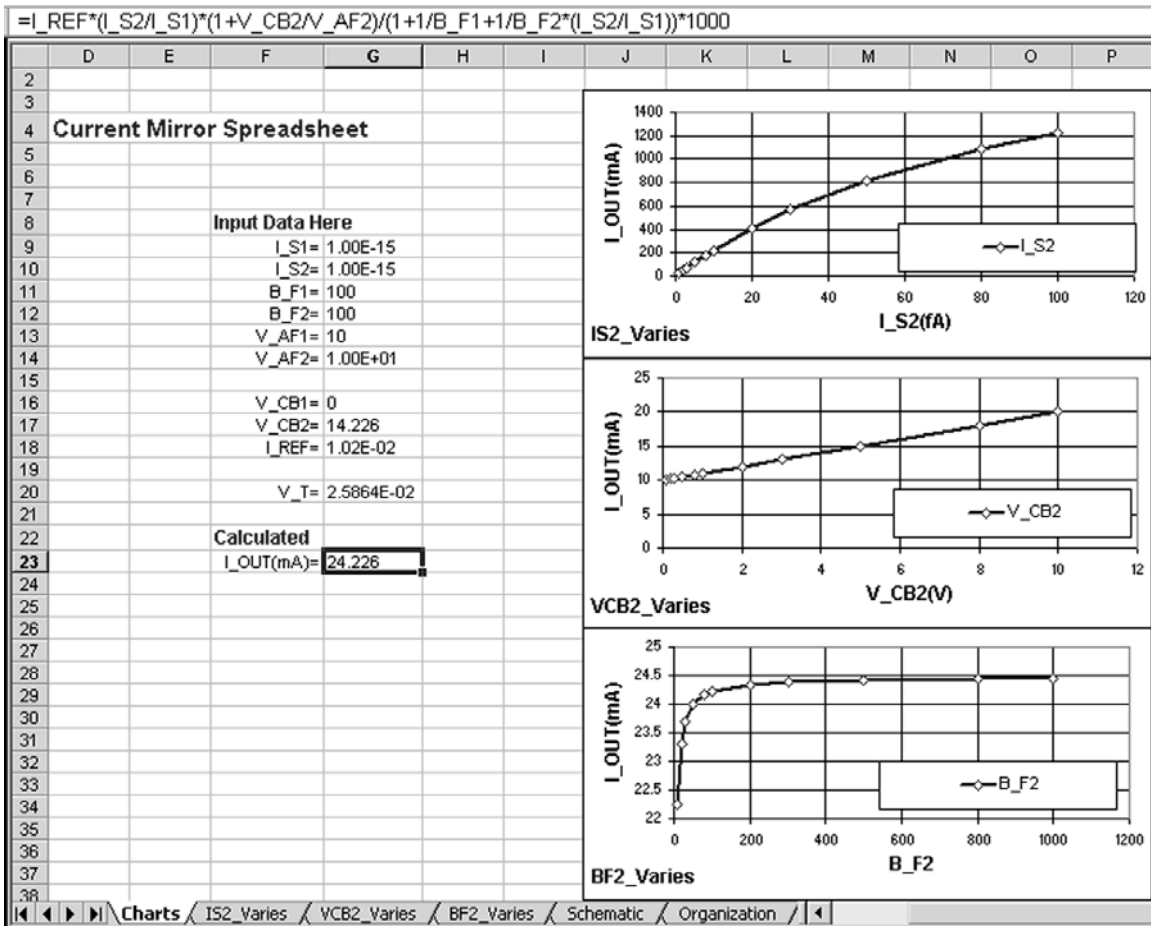


FIGURE 5 CHARTS worksheet; the formula you must derive is in the formula box

**Verification of spreadsheet**

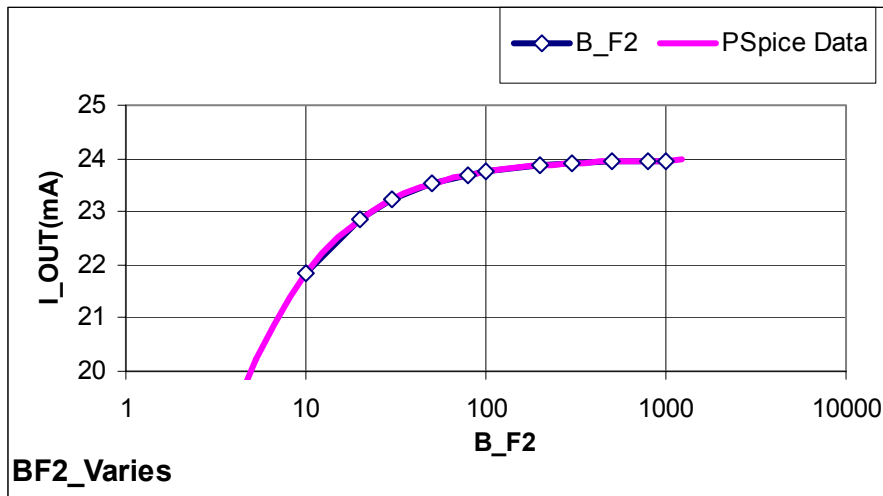
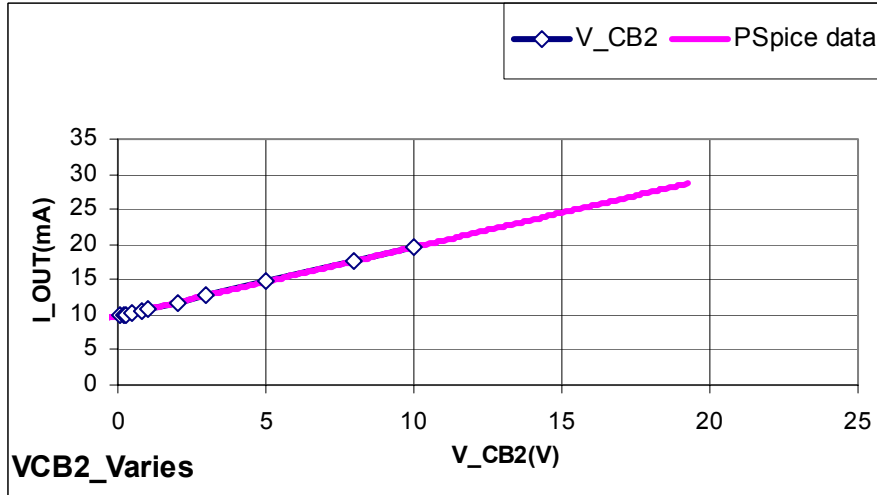


FIGURE 6 Comparison with PSpice for case shown in Figure 7


PARAMETERS:

IS1 = 1fA      IS2 = 1fA  
VAF1 = 10V    VAF2 = 10V  
BF1 = 100      BF2 = 100

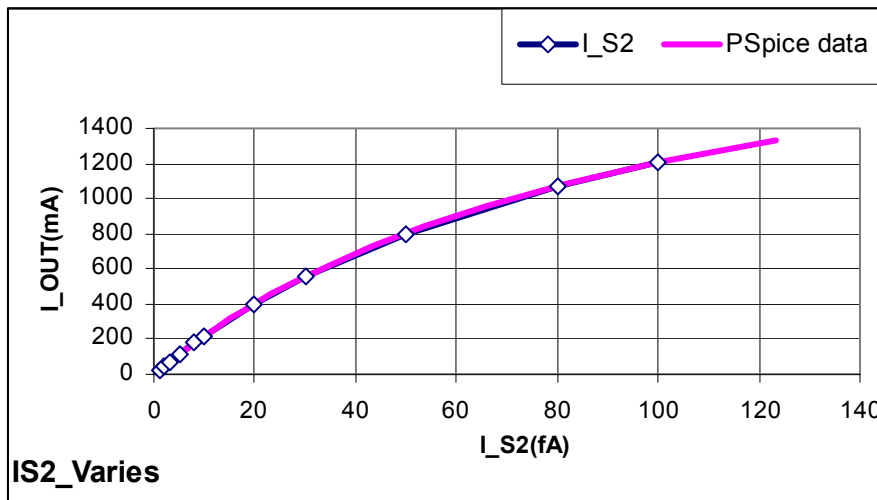**FIGURE 7**  
Parameters for Figure 6 except one parameter is swept

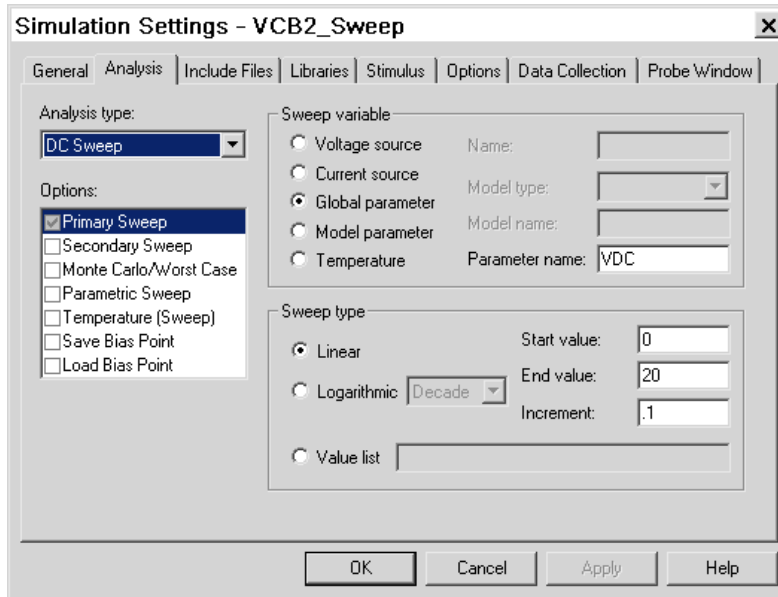


**FIGURE 8**  
Comparison with PSpice for case shown in Figure 7

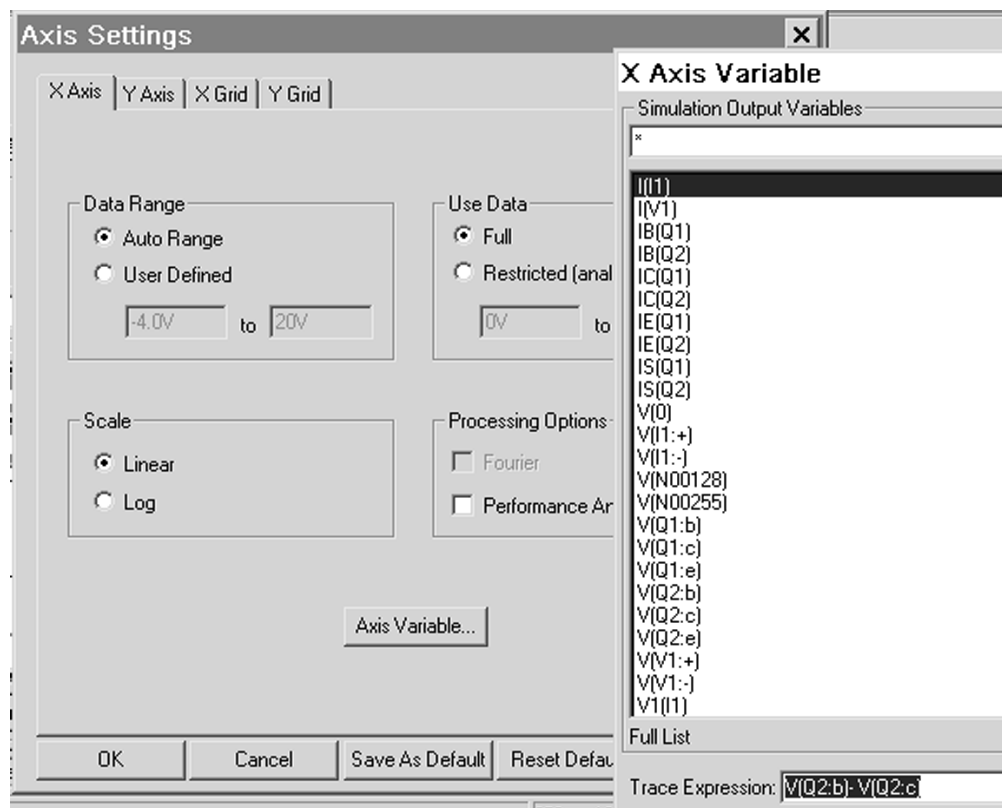


**FIGURE 9**  
Comparison with PSpice for case shown in Figure 7

The comparisons shown in Figure 6, Figure 8 and Figure 9 are made by doing a PSpice DC SWEEP of the parameter involved. For example, for the  $V_{CB}$  sweep, the simulation profile uses the menu of Figure 10, where actually  $V_{DC}$  is the variable swept. Then to get a plot vs.  $V_{BC}$  we use the menu in PROBE shown in Figure 11.

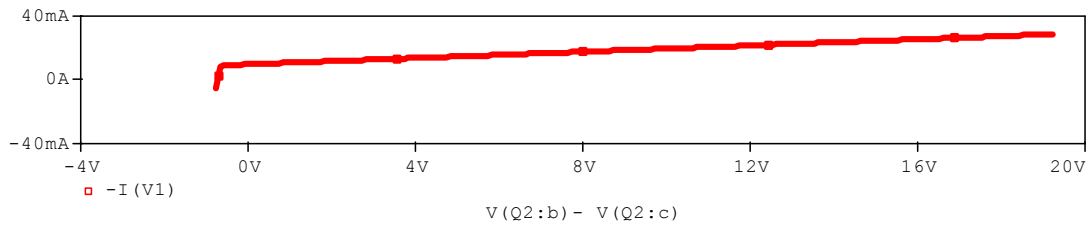


**FIGURE 10**  
DC SWEEP menu for sweeping  $V_{BC}$




**FIGURE 11**  
Using PLOT/AXIS SETTINGS to obtain the AXIS SETTINGS menu, and then hitting the button  
AXIS VARIABLE to allow us to set the x-axis as  $V_{BC}(Q2)$

With the axis set up as indicated, the PROBE plot looks like Figure 12.



**FIGURE 12**  
 PROBE plot based on the menus of Figure 10 and Figure 11

Using Figure 12, we click on the title I(V1) to highlight it and then choose EDIT/COPY from the PROBE toolbar. Next, we go to the worksheet VBC2\_Varies and place the cursor in a convenient location (say cell R7) right click and hit PASTE. The PROBE data is pasted into the spreadsheet. Right click on the chart and select SOURCE DATA/ADD. Fill out the menu to put the PSPICE data on the chart. Click on the LEGEND causing it to highlight. Place the cursor inside the legend and double click on the symbol for the PSPICE data. Move the cursor over the symbol for the PSPICE data and click to cause this symbol to highlight. Then double click to get the FORMAT LEGEND KEY menu of Figure 13. Fill out the menu.

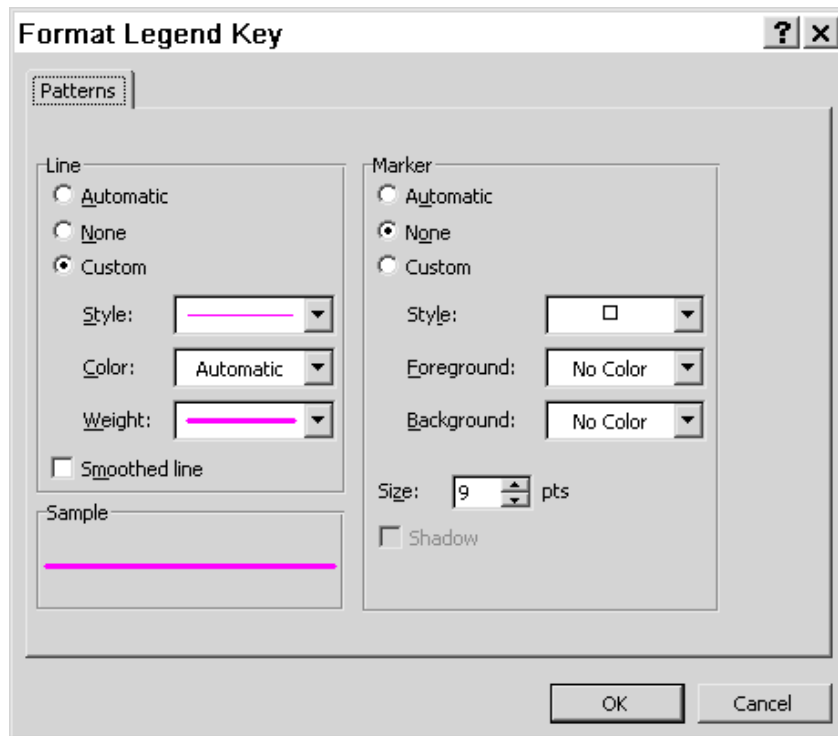

**FIGURE 13**  
 Setting the format for display of the PSPICE data curve

The result is the plot of Figure 8, which shows the calculated data (diamonds) lies on top of the PSPICE results, verifying the formula is working in providing the correct  $V_{BC}$ -dependence of the output current.

### Summary

Here is what you have to deliver:

1. Derivation of  $I_{OUT}$
2. Spreadsheet as described
3. Verification of spreadsheet using PSPICE
4. Report documenting each of the above steps, including detailed derivation