


ECE 274 Digital Logic – Fall 2008


Introduction to Sequential Logic, Basic Storage Element

Digital Design 3.1 – 3.2



Digital Design

Chapter 3: Sequential Logic Design -- Controllers



Slides to accompany the textbook *Digital Design*, First Edition,
by Frank Vahid, John Wiley and Sons Publishers, 2007.
<http://www.ddvahid.com>


Copyright © 2007 Frank Vahid

Instructors of courses requiring Vahid's Digital Design textbook (published by John Wiley and Sons) have permission to modify and use these slides for customary course-related activities, subject to keeping this copyright notice in place and unmodified. These slides may be posted as [annotated pdf](#) versions on publicly-accessible course websites. PowerPoint source (or pdf with animations) may [not](#) be posted to publicly-accessible websites, but may be posted for students on internal protected sites or distributed directly to students by other electronic means. Instructors may make printouts of the slides available to students for a reasonable photocopying charge, without incurring royalties. Any other use requires explicit permission. Instructors may obtain PowerPoint source or obtain special use permissions from Wiley – see <http://www.AbVahid.com> for information.


Sequential Logic Design Introduction

3.1

- Sequential circuit
 - Output depends not just on present inputs (as in combinational circuit), but on past sequence of inputs
 - Stores bits, also known as having “state”
 - Simple example: a circuit that counts up in binary



Combinational digital circuit

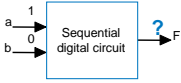

Sequential digital circuit


Must know sequence of past inputs to know output

3

Sequential Logic Design Example Needing Bit Storage

3.2


- Flight attendant call button
 - Press call: light turns on
 - **Stays on** after button released
 - Press cancel: light turns off
 - Logic gate circuit to implement this?




Call
Cancel

Q

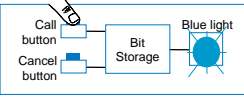
Doesn't work. Q=1 when Call=1, but doesn't stay 1 when Call returns to 0
Need some form of "feedback" in the circuit



1. Call button pressed – light turns on

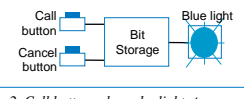

2. Call button released – light stays on

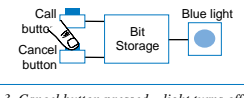

3. Cancel button pressed – light turns off


4

Sequential Logic Design

First attempt at Bit Storage

- We need some sort of feedback

 - Does circuit on the right do what we want?
 - No: Once Q becomes 1 (when S=1), Q stays 1 forever – no value of S can bring Q back to 0




5

Sequential Logic Design

Bit Storage Using an SR Latch

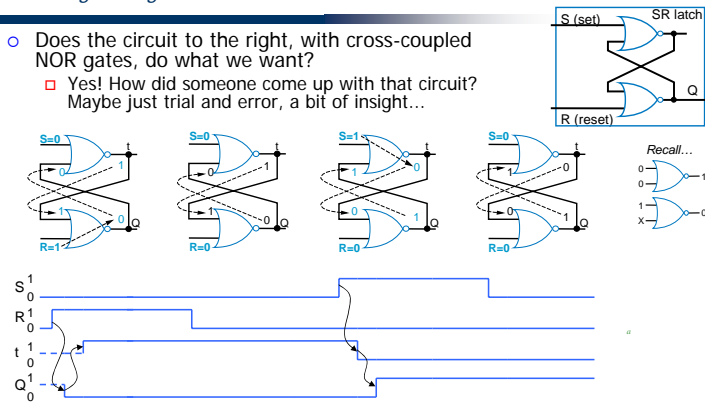- Does the circuit to the right, with cross-coupled NOR gates, do what we want?
 - Yes! How did someone come up with that circuit? Maybe just trial and error, a bit of insight...



6


Sequential Logic Design

Simple Example Using SR Latch for Bit Storage

- SR latch can serve as bit storage in previous example of flight-attendant call button

- Call=1 : sets Q to 1
 - Q stays 1 even after Call=0
 - Cancel=1 : resets Q to 0

- But, there's a problem...

 


7

Sequential Logic Design

SR Latch

- What value with the output Q have at the indicated time?

- 1
- 0
- Neither
- Either

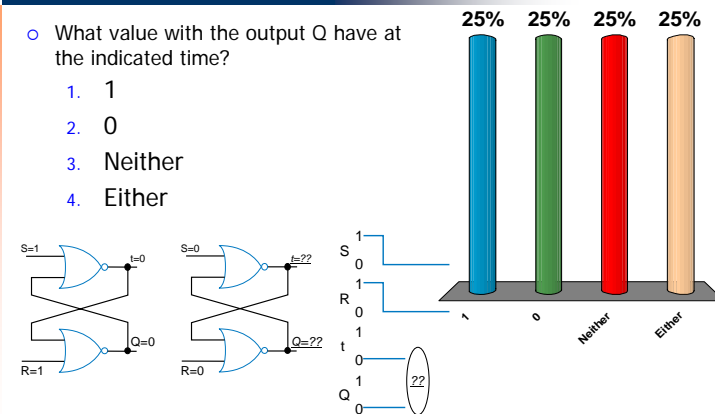


8

Sequential Logic Design

Problem with SR Latch

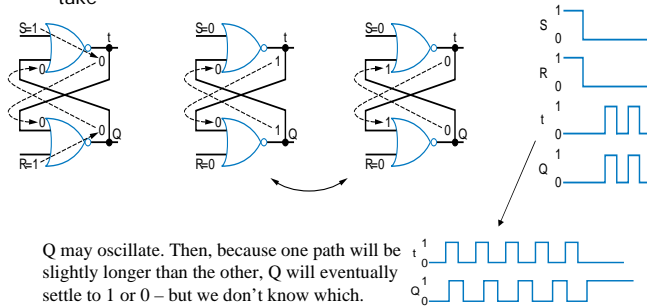Problem

- If $S=1$ and $R=1$ simultaneously, we don't know what value Q will take




9

Sequential Logic Design

Problem with SR Latch

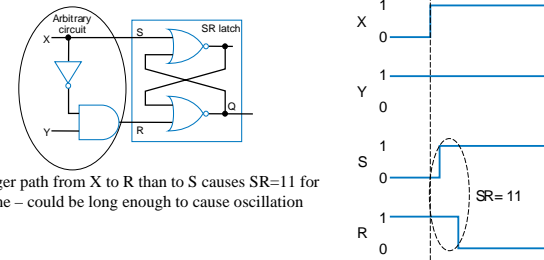- Problem not just one of a user pressing two buttons at same time
- Can also occur even if SR inputs come from a circuit that supposedly never sets $S=1$ and $R=1$ at same time

- But does, due to different delays of different paths,




10

Sequential Logic Design

Solution: Level-Sensitive SR Latch

Add enable input "C" as shown

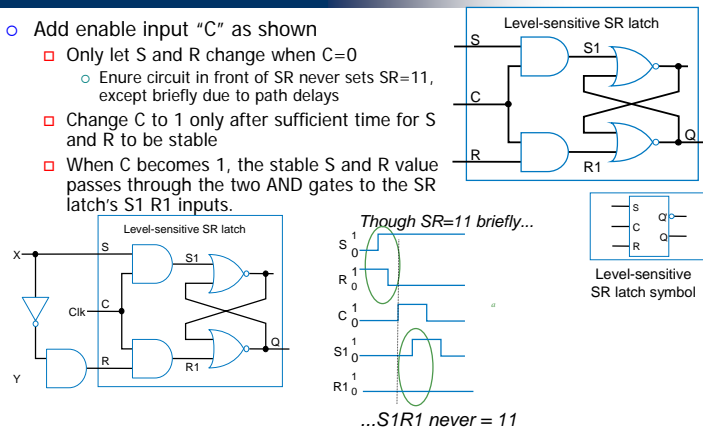- Only let S and R change when $C=0$
 - Ensure circuit in front of SR never sets $SR=11$, except briefly due to path delays
- Change C to 1 only after sufficient time for S and R to be stable
- When C becomes 1, the stable S and R value passes through the two AND gates to the SR latch's $S1$ $R1$ inputs.





11

Sequential Logic Design

Clock Signals for a Latch

How do we know when it's safe to set $C=1$?


- Most common solution - make C pulse up/down
 - $C=0$: Safe to change X, Y
 - $C=1$: Must *not* change X, Y
 - We'll see how to ensure that later
- Clock** signal -- Pulsing signal used to enable latches
 - Because it ticks like a clock
- Sequential circuit whose storage components all use clock signals: **synchronous** circuit
 - Most common type
 - Asynchronous circuits - important topic, but left for advanced course

  

12

Sequential Logic Design

Clock Signal Terminology

 

- Clock period
 - ▣ Time interval between pulses
 - Above signal: period = 20 ns
- Clock cycle
 - ▣ One such time interval
 - Above signal shows 3.5 clock cycles
- Clock frequency
 - ▣ 1/period
 - Above signal: frequency = $1 / 20 \text{ ns} = 50 \text{ MHz}$
 - $1 \text{ Hz} = 1/\text{s}$




Freq	Period
100 GHz	0.01 ns
10 GHz	0.1 ns
1 GHz	1 ns
100 MHz	10 ns
10 MHz	100 ns

13

Sequential Logic Design

Level-Sensitive D Latch

   - SR latch requires careful design to ensure $SR=11$ never occurs
- D latch relieves designer of that burden
 - ▣ Inserted inverter ensures R always opposite of S




14

Sequential Logic Design

 Problem with Level-Sensitive D Latch

- D latch still has problem (as does SR latch)
 - ▣ When $C=1$, through how many latches will a signal travel?
 - ▣ Depends on for how long $C=1$
 - Clk_A -- signal may travel through multiple latches
 - Clk_B -- signal may travel through fewer latches
 - ▣ Hard to pick C that is just the right length
 - Can we design bit storage that only stores a value on the rising edge of a clock signal?




15


Sequential Logic Design

D Flip-Flop

- **Flip-flop:** Bit storage that stores on clock edge, not level
- One design -- master-servant
 - ▣ Two latches, output of first goes to input of second, master latch has inverted clock signal
 - ▣ So master loaded when $C=0$, then servant when $C=1$
 - ▣ When C changes from 0 to 1, master disabled, servant loaded with value that was at D just before C changed -- i.e., value at D during rising edge of C

 

 
Note:
Hundreds of different flip-flop designs exist



16

Sequential Logic Design

D Flip-Flop

 


17

Sequential Logic Design

D Flip-Flop

 - Solves problem of not knowing through how many latches a signal travels when $C=1$
 - In figure below, signal travels through exactly one flip-flop, for Clk_A or Clk_B
 - Why? Because on rising edge of Clk, all four flip-flops are loaded simultaneously -- then all four no longer pay attention to their input, until the next rising edge. Doesn't matter how long Clk is 1.




18

Sequential Logic Design

D Latch vs. D Flip-Flop

 
- Latch is level-sensitive: Stores D when $C=1$
- Flip-flop is edge triggered: Stores D when C changes from 0 to 1
 - Saying "level-sensitive latch," or "edge-triggered flip-flop," is redundant
 - Two types of flip-flops -- rising or falling edge triggered.
- Comparing behavior of latch and flip-flop:



19

Sequential Logic Design

Bit Storage Summary

 

Feature: $S=1$ sets Q to 1, $R=1$ resets Q to 0. Problem: $SR=11$ yield undefined Q .

Feature: S and R only have effect when $C=1$. We can design outside circuit so $SR=11$ never happens when $C=1$. Problem: avoiding $SR=11$ can be a burden.

Feature: SR can't be 11 if D is stable before and while $C=1$, and will be 11 for only a brief glitch even if D changes while $C=1$. Problem: $C=1$ too long propagates new values through too many latches: too short may not enable a store.

Feature: Only loads D value present at rising clock edge, so values can't propagate to other flip-flops during same clock cycle. Tradeoff: uses more gates internally than D latch, and requires more external gates than SR -- but gate count is less of an issue today.

20

Sequential Logic Design

Basic Register

- Typically, we store multi-bit items
 - e.g., storing a 4-bit binary number
- **Register**: multiple flip-flops sharing clock signal
 - From this point, we'll use registers for bit storage
 - No need to think of latches or flip-flops
 - But now you know what's inside a register

