

ECE 274 Digital Logic – Fall 2008

Sequential Logic Design – Controllers

Digital Design 3.3



Digital Design

Chapter 3: Sequential Logic Design -- Controllers

Slides to accompany the textbook *Digital Design*, First Edition,
by Frank Vahid, John Wiley and Sons Publishers, 2007.
<http://www.ddvahid.com>



Copyright © 2007 Frank Vahid


Instructors of courses requiring Vahid's Digital Design textbook (published by John Wiley and Sons) have permission to modify and use these slides for customary course-related activities, subject to keeping this copyright notice in place and unmodified. These slides may be posted as [annotated pdf](#) versions on publicly-accessible course websites. PowerPoint source (or pdf with animations) may [not](#) be posted to publicly-accessible websites, but may be posted for students on internal protected sites or distributed directly to students by other electronic means. Instructors may make printouts of the slides available to students for a reasonable photocopying charge, without incurring royalties. Any other use requires explicit permission. Instructors may obtain PowerPoint source or obtain special use permissions from Wiley -- see <http://www.AhVahid.com> for information.

Sequential Logic Design

Describing Behavior of Sequential Circuit: FSM

Finite-State Machine (FSM)

- A way to describe desired behavior of sequential circuit
 - Akin to Boolean equations for combinational behavior
- List states, and transitions among states
 - Example: Make x change toggle (0 to 1, or 1 to 0) every clock cycle
 - Two states: "Off" ($x=0$), and "On" ($x=1$)
 - Transition from Off to On, or On to Off, on rising clock edge
 - Arrow with no starting state points to initial state (when circuit first starts)

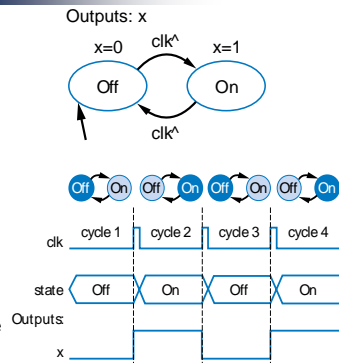


3

Sequential Logic Design

FSM Example: Three-Cycles High Laser Timer

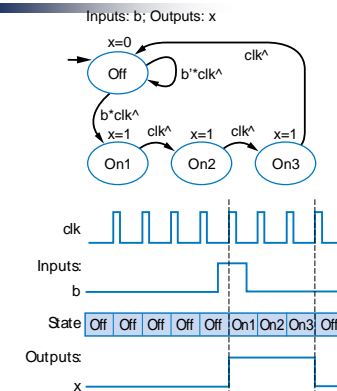- Three Cycle High Laser Timer
 - Turn on laser for three cycles whenever button is pressed
- FSM needs four states
 - Wait in *Off* state while b is 0 (b')
 - When b is 1 (and rising clock edge), transition to *On1*
 - Sets $x=1$
 - On next two clock edges, transition to *On2*, then *On3*, which also set $x=1$
 - So $x=1$ for three cycles after button pressed




4

Sequential Logic Design

FSM Simplification: Rising Clock Edges Implicit

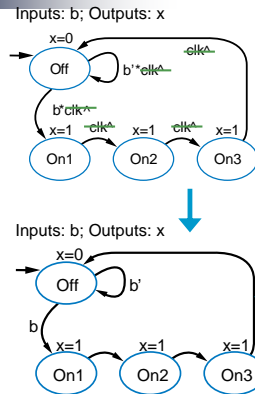- Showing rising clock on every transition: cluttered
 - Make implicit -- assume every edge has rising clock, even if not shown
 - What if we wanted a transition *without* a rising edge
 - We don't consider such asynchronous FSMs -- less common, and advanced topic
 - Only consider **synchronous** FSMs -- rising edge on *every* transition




Note: Transition with no associated condition thus transitions to next state on next clock cycle

5

Sequential Logic Design

FSM Definition

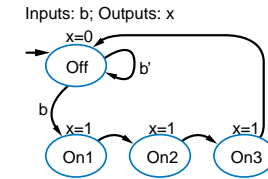- FSM consists of
 - Set of states
 - Ex: {Off, On1, On2, On3}
 - Set of inputs, set of outputs
 - Ex: Inputs: {x}, Outputs: {b}
 - Initial state
 - Ex: "Off"
 - Set of transitions
 - Describes next states
 - Ex: Has 5 transitions
 - Set of actions
 - Sets outputs while in states
 - Ex: $x=0$, $x=1$, $x=1$, and $x=1$



We often draw FSM graphically, known as **state diagram**


Can also use table (state table), or textual languages

6

Sequential Logic Design

FSM Example: Secure Car Key

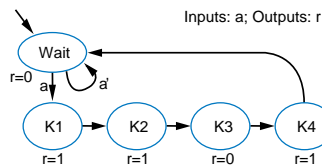- Many new car keys include tiny computer chip
 - When car starts, car's computer (under engine hood) requests identifier from key
 - Key transmits identifier
 - If not, computer shuts off car
- FSM
 - Wait until computer requests ID ($a=1$)
 - Transmit ID (in this case, 1101)






7

Sequential Logic Design

FSM Example: Secure Car Key (cont.)

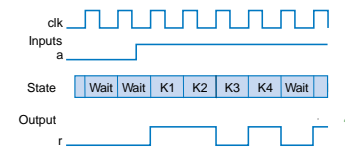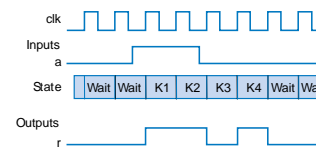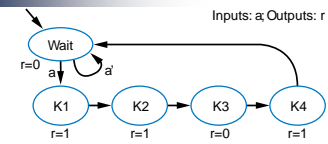- Nice feature of FSM
 - Can evaluate output behavior for different input sequence
 - Timing diagrams show states and output values for different input waveforms




8

Sequential Logic Design

FSM Example: Code Detector

- What is the state in the FSM in at the indicated time?

- K1
- K2
- K3
- K4

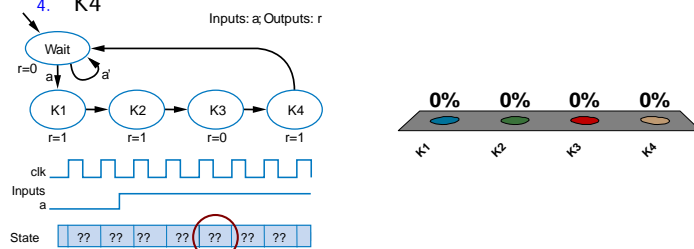


9

Sequential Logic Design


FSM Example: Code Detector

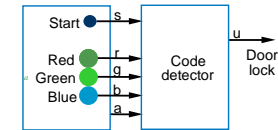- Unlock door ($u=1$) only when buttons pressed in sequence:
 - start, then red, blue, green, red
- Input from each button: s, r, g, b, a
 - Also, output a indicates that some colored button pressed



- FSM

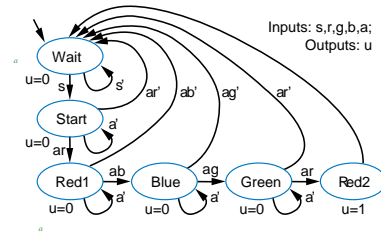- Wait for start ($s=1$) in "Wait"
- Once started ("Start")
 - If see red, go to "Red1"
 - Then, if see blue, go to "Blue"
 - Then, if see green, go to "Green"
 - Then, if see red, go to "Red2"
 - In that state, open the door ($u=1$)
- Wrong button at any step, return to "Wait", without opening door




10

Sequential Logic Design

FSM Example: Code Detector

- Can you trick this FSM to open the door, without knowing the code?


- Yes
- No
- Not sure

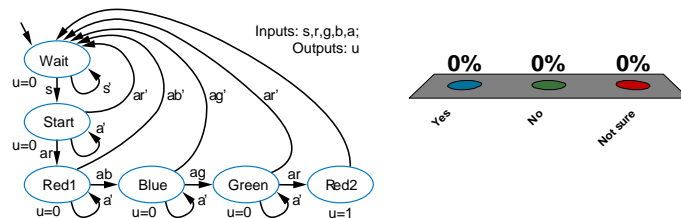

11

Sequential Logic Design

Improve FSM for Code Detector

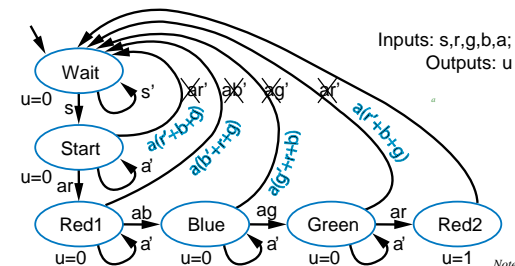

- New transition conditions detect if wrong button pressed, returns to "Wait"
- FSM provides formal, concrete means to accurately define desired behavior

12

Sequential Logic Design

Standard Controller Architecture

How implement FSM as sequential circuit?

- Use standard architecture
 - State register -- to store the present state
 - Combinational logic -- to compute outputs, and next state
 - For laser timer FSM
 - 2-bit state register, can represent four states
 - Input b, output x
- Known as *controller*

