

ECE 274 Digital Logic – Fall 2008



Datapath Component Design using Verilog

Verilog for Digital Design Ch. 3



Multifunction Register Behavior

  - Previously-considered register loaded on every clock cycle
- Now consider register with control inputs, such as load or shift
 - Could describe structurally
 - Four flip-flops, four muxes, and some combinational logic (to convert control inputs to mux select inputs)
 - We'll describe behaviorally



Ld	Shr	Shl	Operation
0	0	0	Maintain present value
0	0	1	Shift left
0	1	0	Shift right
0	1	1	Shift right – Shr has priority over Shl
1	0	0	Parallel load
1	0	1	Parallel load – Ld has priority
1	1	0	Parallel load – Ld has priority
1	1	1	Parallel load – Ld has priority

Ld	Shr	Shl	Operation
0	0	0	Maintain value
0	0	1	Shift left
0	1	X	Shift right
1	X	X	Parallel load

Compact register operation table, clearly showing priorities

Multifunction Register Behavior

- Use if-else-if construct
 - else-if parts ensure correct priority of control inputs
 - Rst has first priority, then Ld, then Shr, and finally Shl
- Shift by assigning each bit
 - Recall that statement order doesn't matter
- Use reg variable R for storage
 - Best not to try to use port Q – good practice dictates not reading a module's output ports from within a module
- Use continuous assignment to update Q when R changes
 - Identifier on left of "=" must be a net, not a variable

```

`timescale 1 ns/1 ns
module MfReg4(I, Q, Ld, Shr, Shl, Shr_in, Shl_in, Clk, Rst);
    input [3:0] I;
    output [3:0] Q;
    input Ld, Shr, Shl, Shr_in, Shl_in;
    input Clk, Rst;
    reg [3:0] R;

    always @(posedge Clk) begin
        if (Rst == 1)
            R <= 4'b0000;
        else if (Ld == 1)
            R <= I;
        else if (Shr == 1) begin
            R[3] <= Shr_in; R[2] <= R[3];
            R[1] <= R[2]; R[0] <= R[1];
        end
        else if (Shl == 1) begin
            R[0] <= Shl_in; R[1] <= R[0];
            R[2] <= R[1]; R[3] <= R[2];
        end
    end
    assign Q = R;
endmodule
    
```

Ld	Shr	Shl	Operation
0	0	0	Maintain value
0	0	1	Shift left
0	1	X	Shift right
1	X	X	Parallel load


v1d3_ch4_MfReg4.v

Multifunction Register Behavior

- Testbench should test numerous possible loads and shifts
 - Testbench shown is brief
 - Resets register to 0000
 - Loads 1111
 - Shifts right, shifting in 0
 - Continues shifting right
 - Eventually register is 0000

```

 // Clock Procedure
...
// Vector Procedure
initial begin
    Rst_s <= 1;
    I_s <= 4'b0000;
    Ld_s <= 0; Shr_s <= 0; Shl_s <= 0;
    Shr_in_s <= 0; Shl_in_s <= 0;
    @(posedge Clk_s);
    #5 Rst_s <= 0;
    I_s <= 4'b1111; Ld_s <= 1;
    @(posedge Clk_s);
    #5 Ld_s <= 0; Shr_s <= 1;
    // Good testbench needs more vectors
end
endmodule
    
```



Multifunction Register Behavior

- Question: Does the shown description, with Q declared as a reg, and "Q <= R;" as the last statement, correctly describe the register?

- Answer: No. Q gets the present value of R, not the scheduled value.

```

`timescale 1 ns/1 ns
module MReg4(I, Q, Ld, Shr, Shl, Shr_in, Shl_in, Clk, Rst);
    input [3:0] I;
    output [3:0] Q;
    reg [3:0] Q;
    input Ld, Shr, Shl, Shr_in, Shl_in;
    input Clk, Rst;

    reg [3:0] R;

    always @(posedge Clk) begin
        if (Rst == 1)
            R <= 4'b0000;
        else if (Ld == 1)
            R <= I;
        else if (Shr == 1) begin
            R[3] <= Shr_in; R[2] <= R[3];
            R[1] <= R[2]; R[0] <= R[1];
        end
        else if (Shl == 1) begin
            R[0] <= Shl_in; R[1] <= R[0];
            R[2] <= R[1]; R[3] <= R[2];
        end
        Q <= R;
    end
endmodule
v1dd_ch4_MReg4Wrong.v
    
```

5

Multifunction Register Behavior

- Question: Does the shown description, with Q declared as a reg, and "Q <= R;" as the last statement, correctly describe the register?

- Answer: No. Q gets the present value of R, not the scheduled value.
 - Q thus lags behind R by 1 cycle

```

always @(posedge Clk) begin
    if (Rst == 1)
        R <= 4'b0000;
    else if (Ld == 1)
        R <= I;
    else if (Shr == 1) begin
        R[3] <= Shr_in; R[2] <= R[3];
        R[1] <= R[2]; R[0] <= R[1];
    end
    else if (Shl == 1) begin
        R[0] <= Shl_in; R[1] <= R[0];
        R[2] <= R[1]; R[3] <= R[2];
    end
    Q <= R;
end
v1dd_ch4_MReg4Wrong.v
    
```

Should have become 0000 on the first clock cycle

6

Common Pitfall Not Using Begin-End Block in If Statement

- For more compact code, designers sometimes don't use begin-end block for if statement having just one sub-statement
 - As in our register description
- Problem occurs if one adds another sub-statement later without remembering to add begin-end block
- Solution – Always use begin-end block in if statement

```

always @(posedge Clk) begin
    if (Rst == 1)
        R <= 4'b0000;
    ↓ Later
    always @(posedge Clk) begin
        if (Rst == 1)
            R <= 4'b0000;
            ↓ Later
            $display("Reset done.");
    Displays even if Rst not 1
    always @(posedge Clk) begin
        if (Rst == 1) begin
            R <= 4'b0000;
            end
            ↓ Later
            always @(posedge Clk) begin
                if (Rst == 1) begin
                    R <= 4'b0000;
                    $display("Reset done.");
                end
            end
    
```

7

4-Bit Adder

- 4-bit adder adds two 4-bit binary inputs A and B, sets 4-bit output S
- Could describe structurally
 - Carry-ripple: 4 full-adders
- Behaviorally
 - Simply: S <= A + B
 - "always" procedure sensitive to A and B
 - Adder is combinational – must include all inputs in sensitivity list
 - Note: procedure resumes if any bit in either vector changes

```

`timescale 1 ns/1 ns
module Add4(A, B, S);
    input [3:0] A, B;
    output [3:0] S;
    reg [3:0] S;

    always @(A, B) begin
        S <= A + B;
    end
endmodule
v1dd_ch4_Add4.v
    
```

8

4-Bit Adder

- o "+" is built-in arithmetic operator for addition
 - Built-in arithmetic operators include:
 - o + : addition
 - o - : subtraction
 - o * : multiplication
 - o / : division
 - o % : modulus
 - o ** : power ("a ** b" is a raised to the power of b)
 - The operators are intentionally defined to be similar to those in the C programming language

```

`timescale 1 ns/1 ns
module Add4(A, B, S);
    input [3:0] A, B;
    output [3:0] S;
    reg [3:0] S;

    always @(A, B) begin
        S <= A + B;
    end
endmodule
    
```

v1dd_ch4_Add4.v

9

4-Bit Adder Testbench

- o Standard testbench format
 - Needs more vectors than shown
 - Should also be self-checking
- o Simulation yields
 - 0011 + 0001 → S_s is 0100
 - o 3 + 1 = 4
 - 1100 + 0011 → S_s is 1111
 - o 12 + 3 = 15
 - 5 + 2 → S_s is 0111
 - o Last vector shows use of decimal constant rather than binary

```

`timescale 1 ns/1 ns
module Testbench();
    reg [3:0] A_s, B_s;
    wire [3:0] S_s;

    Add4 CompToTest(A_s, B_s, S_s);

    initial begin
        A_s <= 4'b0011; B_s <= 4'b0001;
        #10;
        A_s <= 4'b1100; B_s <= 4'b0011;
        #10;
        A_s <= 4'd5; // Equivalent to 4'b0101
        B_s <= 4'd2; // Equivalent to 4'b0010
        // Good testbench needs more vectors
    end
endmodule
    
```

v1dd_ch4_Add4TB.v

10

4-Bit Adder with Carry-In and Carry-Out

- o Adders have carry-in and carry-out bits
 - Extend Add4 with Ci, Co
- o S <= A + B + Ci
 - Yields correct sum
 - o "+" operator handles different bit-widths – extends Ci to 4 bits, padded on left with 0s
 - But carry-out?
 - o S is only 4 bits; Co is a fifth bit
- o Solution – Do 5-bit add, separate fifth bit (carry-out) from lower four
 - Uses concatenate operator "{" }
 - Uses blocking assignment "="
 - Both to be described now

```

`timescale 1 ns/1 ns
module Add4wCarry(A, B, Ci, S, Co);
    input [3:0] A, B;
    input Ci;
    output [3:0] S;
    reg [3:0] S;
    output Co;
    reg Co;

    reg [4:0] A5, B5, S5;

    always @(A, B, Ci) begin
        A5 = {1'b0, A}; B5 = {1'b0, B};
        S5 = A5 + B5 + Ci;
        S <= S5[3:0];
        Co <= S5[4];
    end
endmodule
    
```

v1dd_ch4_Add4wCarry.v

11

4-Bit Adder with Carry-In and Carry-Out Concatenation Operator

- o Concatenation operator "{" }"
 - Joins bits from two or more expressions
 - o Expressions separated by commas within { }
 - {1b'0, A} → 5-bit value:
 - o "0 A[3] A[2] A[1] A[0]"
 - {1b'0, 4b'0011} → "00011"
 - {2b'11, 2b'00, 2b'01} → "110001"

```

`timescale 1 ns/1 ns
module Add4wCarry(A, B, Ci, S, Co);
    input [3:0] A, B;
    input Ci;
    output [3:0] S;
    reg [3:0] S;
    output Co;
    reg Co;

    reg [4:0] A5, B5, S5;

    always @(A, B, Ci) begin
        A5 = {1'b0, A}; B5 = {1'b0, B};
        S5 = A5 + B5 + Ci;
        S <= S5[3:0];
        Co <= S5[4];
    end
endmodule
    
```

v1dd_ch4_Add4wCarry.v

12

4-Bit Adder with Carry-In and Carry-Out Blocking and Non Blocking Assignment Statements

- Blocking assignment statement
 - Uses "="
 - Variable is updated before execution proceeds
 - Like variable update in C language
- Non-blocking assignment statement
 - Uses "<="
 - Update is scheduled but doesn't occur until later in simulation cycle
 - What we've been using until now
- Guideline
 - Use blocking assignment when computing intermediate values

```

`timescale 1 ns/1 ns
module Add4wCarry(A, B, Ci, S, Co);
    input [3:0] A, B;
    input Ci;
    output [3:0] S;
    reg [3:0] S;
    output Co;
    reg Co;

    reg [4:0] A5, B5, S5;

    always @(A, B, Ci) begin
        A5 = {1'b0, A}; B5 = {1'b0, B};
        S5 = A5 + B5 + Ci;
        S <= S5[3:0];
        Co <= S5[4];
    end
endmodule
    
```

v1dd_ch4_Add4wCarry.v

13

4-Bit Adder with Carry-In and Carry-Out

- A5 = {1'b0, A} → 5-bit version of A
- B5 = {1'b0, B} → 5-bit version of B
- S5 = A5 + B5 + Ci → 5-bit sum
- Note:
 - Blocking assignment "=" means that above values are updated immediately, rather than being scheduled for update later. Thus, subsequent statements use updated values
- S <= S5[3:0] → 4-bit S gets 4 low bits of S5
 - Part selection used to access multiple bits within vector
 - Desired high and low bit positions specified within [] separated by :
- Co <= S5[4] → Co gets 5th bit of S5, which corresponds to the carry-out of A+B+Ci

```

`timescale 1 ns/1 ns
module Add4wCarry(A, B, Ci, S, Co);
    input [3:0] A, B;
    input Ci;
    output [3:0] S;
    reg [3:0] S;
    output Co;
    reg Co;

    reg [4:0] A5, B5, S5;

    always @(A, B, Ci) begin
        A5 = {1'b0, A}; B5 = {1'b0, B};
        S5 = A5 + B5 + Ci;
        S <= S5[3:0];
        Co <= S5[4];
    end
endmodule
    
```

v1dd_ch4_Add4wCarry.v

14

4-Bit Adder with Carry-In and Carry-Out Alternative Description

- A more compact description is possible
- Use concatenation on the left side of assignment
 - {Co, S} <= A + B + Ci
 - Left side thus 5 bits wide
- Rule
 - For the + operator, all operands extended to width of widest operand, including left side
 - Left side is 5 bits → A, B, and Ci all extended to 5 bits, left padded with 0s
 - E.g., A: 0011, B: 0001, Ci: 1 → 00011+00001+00000 yields 00100
 - Co gets first 0, S gets 0100
- Though longer, previous description synthesizes to same circuit
 - reg [4:0] A5, B5, S5; – Synthesize into wires

```

`timescale 1 ns/1 ns
module Add4wCarry(A, B, Ci, S, Co);
    input [3:0] A, B;
    input Ci;
    output reg [3:0] S;
    output reg Co;

    always @(A, B, Ci) begin
        {Co, S} <= A + B + Ci;
    end
endmodule
    
```

v1dd_ch4_Add4wCarry2.v

15

4-Bit Adder with Carry-In and Carry-Out Testbench

- Similar to earlier adder testbench, with Co_s
- Needs more vectors, should also be made self-checking

```

`timescale 1 ns/1 ns
module Testbench();
    reg [3:0] A_s, B_s;
    reg Ci_s;
    wire [3:0] S_s;
    wire Co_s;

    Add4wCarry CompToTest(A_s, B_s, Ci_s, S_s, Co_s);

    initial begin
        A_s <= 4'b0011; B_s <= 4'b0001;
        Ci_s <= 0;
        #10;
        A_s <= 4'b1100; B_s <= 4'b0011;
        Ci_s <= 1;
        #10;
        A_s <= 4'd5; // Equivalent to 4'b0101
        B_s <= 4'd2; // Equivalent to 4'b0010
        // Good testbench needs more vectors
    end
endmodule
    
```


v1dd_ch4_Add4wCarryTB.v

16

4-Bit Shift Register

Shift Register


- Consider a 4-bit shift register with only a right shift control input
 - Either retains its current value or shift the register contents right
- Can again describe register behaviorally
 - Perform shifting bit by bit, as in previous multifunction register example
- Could also use concatenation
 - Replace bit-by-bit assignment with single statement using concatenation
 - $R \leftarrow \{Shr_in, R[3], R[2], R[1]\}$
- What if the register has 32-bits?
 - Both bit-by-bit assignment and concatenation become tedious for large items
 - Could lead to errors

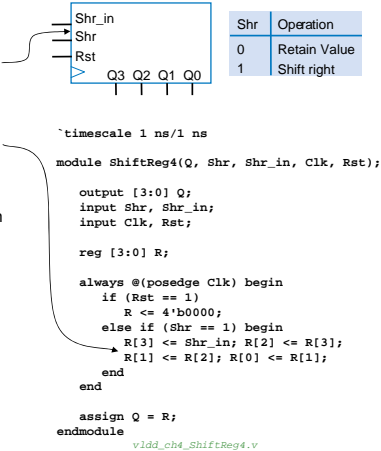

17

32-Bit Shift Register

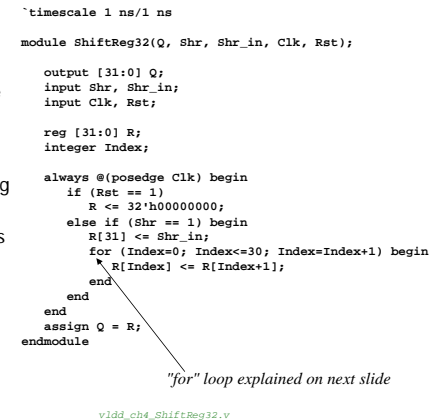
- Now consider a 32-bit shift register with right shift control input
 - Both bit by bit assignment and concatenation become cumbersome, tedious, and error prone
- Solution:
 - Use loop to perform shifting
- Loop
 - Defines a set of statements that will be repeatedly executed some number of times
 - Loop parameters control execution of loop



18

32-Bit Shift Register for loop statement


- for loop statement
 - Typically defines loop that executes specified number of times
- Typically involves:
 - Index variable declaration
 - Index variable initialization
 - executed only once
 - Loop condition checked
 - Usually involves index
 - Loop exits if not true
 - Loop body statement executed
 - Usually a begin-end block
 - Followed by execution of index variable update
- Loop thus assigns every R bit to next higher bit
 - Last bit handled by statement $R[31] \leftarrow Shr_in$; → Assign highest bit to shift input

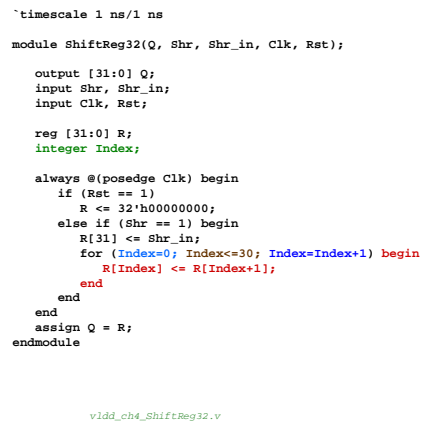

19

32-Bit Shift Register Integer Data Type

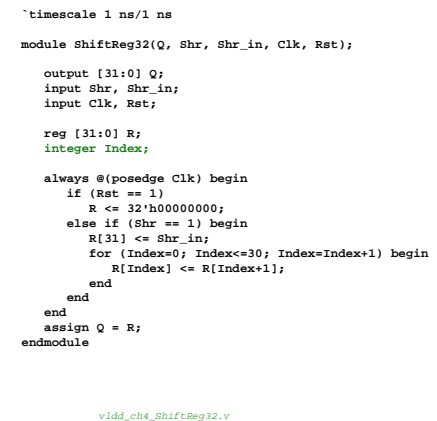- Index declared as integer
- integer
 - Another variable data type
 - Previous was "reg"
 - Bit or vector of bits
 - Integer can be negative or positive (signed), 32-bits
 - Use when it makes code clearer
 - Especially if item not destined to become a physical register



20

32-Bit Shift Register Relational and Logic Operators

- "<=" – built-in relational operator
 - Looks same as non blocking assignment – distinguished by how operator is used
- Built-in relational operators
 - > : greater than
 - < : less than
 - >= : greater than or equal
 - <= : less than or equal

```

`timescale 1 ns/1 ns
module ShiftReg32(Q, Shr, Shr_in, Clk, Rst);
    output [31:0] Q;
    input Shr, Shr_in;
    input Clk, Rst;

    reg [31:0] R;
    integer Index;

    always @(posedge Clk) begin
        if (Rst == 1)
            R <= 32'h00000000;
        else if (Shr == 1) begin
            R[31] <= Shr_in;
            for (Index=0; Index<=30; Index=Index+1) begin
                R[Index] <= R[Index+1];
            end
        end
    end
    assign Q = R;
endmodule
    
```

vldd_ch4_ShiftReg32.v

21

32-Bit Shift Register Relational and Logic Operators

- Built-in logical operators
 - ! : logical negation
 - && : logical AND
 - || : logical OR
- Built-in equality operators
 - == : logical equality
 - != : logical inequality
 - === : logical equality
 - including x and z bits (more on this later)
 - !== : logical inequality
 - including x and z bits (more on this later)

```

`timescale 1 ns/1 ns
module ShiftReg32(Q, Shr, Shr_in, Clk, Rst);
    output [31:0] Q;
    input Shr, Shr_in;
    input Clk, Rst;

    reg [31:0] R;
    integer Index;

    always @(posedge Clk) begin
        if (Rst == 1)
            R <= 32'h00000000;
        else if (Shr == 1) begin
            R[31] <= Shr_in;
            for (Index=0; Index<=30; Index=Index+1) begin
                R[Index] <= R[Index+1];
            end
        end
    end
    assign Q = R;
endmodule
    
```

vldd_ch4_ShiftReg32.v

22

32-Bit Shift Register Testbench

- Testbench
 - Shifting bits individually into the shift register would also be tedious
 - Use for loops to simplify the testbench
- Shift 16 1s into register
 - Set register to shift right with shift input of 1
 - for loop waits 16 clock cycles
 - Loop executes 16 time, each time waiting for rising clock edge
 - Self-check verifies correctly shifted register output
- Shift 16 0s into register
 - for loop waits 16 clock cycles
 - Self-checks again
- Good testbench would have more vectors

```

...
// Vector Procedure
initial begin
    Rst_s <= 1;
    Shr_s <= 0; Shr_in_s <= 0;
    @(posedge Clk_s);
    #5 Rst_s <= 0;
    @(posedge Clk_s);
    #5 Shr_s <= 1; Shr_in_s <= 1;
    for (Index=0; Index<=15; Index=Index+1) begin
        @(posedge Clk_s);
    end
    #5;
    if (Q_s != 32'hFFFF0000)
        $display("Failed Q=FFFF0000");
    Shr_s <= 1; Shr_in_s <= 0;
    for (Index=0; Index<=15; Index=Index+1) begin
        @(posedge Clk_s);
    end
    #5;
    if (Q_s != 32'h0000FFFF)
        $display("Failed Q=0000FFFF");
    Shr_s <= 0;
end
endmodule
    
```

vldd_ch4_ShiftReg32TB.v

23

Testbench with File Input – 32-Bit Shift Register

- Testbench can read test vectors from an input file
 - Compact
 - Allows for easy integration of new test vectors without modifying testbench or recompiling
 - Can define several separate vector files to test different aspects
- File: document located on host computer system, can be read from or written to
 - Verilog has built-in system procedures for files
- Four types of procedures in Verilog
 - Initial and always – already seen
 - Function – Has at least one input argument, returns a value, no time-controlling statements (executes in one simulation time unit)
 - Task – Any number of arguments, no return value, may have time-controlling statements
- Testbench for the 32-Bit shift register reads test vectors from input file
 - Input file specifies bits to be shifted into register
 - Set register to shift right and read input bits from file

```

integer FileId;
reg[8:0] BitChar;

// Vector Procedure
initial begin
    FileId = $fopen("vectors.txt", "r");
    if (FileId == 0)
        $display("Could not open input file.");
    else begin
        Rst_s <= 1;
        Shr_s <= 0; Shr_in_s <= 0;
        @(posedge Clk_s);
        #5 Rst_s <= 0;
        @(posedge Clk_s);
        #5 Shr_s <= 1;
        while ($feof(FileId) == 0) begin
            BitChar = $fgetc(FileId);
            if (BitChar == "1") begin
                Shr_in_s <= 1;
                @(posedge Clk_s);
            end
            else if (BitChar == "0") begin
                Shr_in_s <= 0;
                @(posedge Clk_s);
            end
        end
        $fclose(FileId);
    end
    Shr_s <= 0;
end
endmodule
    
```

file procedures to be described on next slide

vldd_ch4_ShiftReg32TBF1e10.v

24

Testbench with File Input

– System Procedures for Files

- o **\$fopen** – Opens file for access
 - Arguments:
 - File name: "vectors.txt"
 - Access type: "r" means read, "w" write, "a" append
 - Returns integer, used to identify opened file (may be more than one file open at one time); 0 means error
- o **\$feof** – Returns 0 if end of file has not been reached yet
- o **\$fgetc** – Returns next character in file
 - Valid character is 8 bits
 - If error, returns 9-bit value 11111111
 - Thus, variable BitChar is 9 bits, not 8
- o **\$fclose** – Closes previously-opened file

```
integer FileId;
reg[8:0] BitChar;

// Vector Procedure
initial begin
    FileId = $fopen("vectors.txt", "r");
    if (FileId == 0)
        $display("Could not open input file.");
    else begin
        Rst_s <= 1;
        Shr_s <= 0; Shr_in_s <= 0;
        @(posedge Clk_s);
        #5 Rst_s <= 0;
        @(posedge Clk_s);
        #5 Shr_s <= 1;
        while ($feof(FileId) == 0) begin
            BitChar = $fgetc(FileId);
            if (BitChar == "1") begin
                Shr_in_s <= 1;
                @(posedge Clk_s);
            end
            else if (BitChar == "0") begin
                Shr_in_s <= 0;
                @(posedge Clk_s);
            end
        end
        $fclose(FileId);
    end
    Shr_s <= 0;
end
endmodule
```

while loop to be described on next slide
vldd_ch4_ShiftReg32TBFileIO.v

25

Testbench with File Input

– While Loops

- o Uses another form of loop: **while**
 - If **condition** is true, executes loop body statement (usually **begin-end block**)
 - Repeat
- o Both while and for loops are common
 - for loop typically used when number of iterations is known (e.g., loop 16 times)
 - while loop typically used when number of iterations not known

```
integer FileId;
reg[8:0] BitChar;

// Vector Procedure
initial begin
    FileId = $fopen("vectors.txt", "r");
    if (FileId == 0)
        $display("Could not open input file.");
    else begin
        Rst_s <= 1;
        Shr_s <= 0; Shr_in_s <= 0;
        @(posedge Clk_s);
        #5 Rst_s <= 0;
        @(posedge Clk_s);
        #5 Shr_s <= 1;
        while ($feof(FileId) == 0) begin
            BitChar = $fgetc(FileId);
            if (BitChar == "1") begin
                Shr_in_s <= 1;
                @(posedge Clk_s);
            end
            else if (BitChar == "0") begin
                Shr_in_s <= 0;
                @(posedge Clk_s);
            end
        end
        $fclose(FileId);
    end
    Shr_s <= 0;
end
endmodule
```

Entire vector procedure to be described on next slide
vldd_ch4_ShiftReg32TBFileIO.v

26

Testbench with File Input – 32-Bit Register

- o Open file containing test vectors
 - If file failed to open (maybe doesn't exist), display error message
- o Reset register
- o Enable shifting
- o While we haven't read the entire vector file
 - Read next character from file
 - If 1, shift in a 1
 - Set shift input to 1, wait for clock
 - Else if 0, shift in a 0
 - Can't just assign Shr_in_s <= BitChar; one's a bit, one's a 9-bit ASCII encoding of a character
- o When read entire file, close file

```
integer FileId;
reg[8:0] BitChar;


// Vector Procedure
initial begin
    FileId = $fopen("vectors.txt", "r");
    if (FileId == 0)
        $display("Could not open input file.");
    else begin
        Rst_s <= 1;
        Shr_s <= 0; Shr_in_s <= 0;
        @(posedge Clk_s);
        #5 Rst_s <= 0;
        @(posedge Clk_s);
        #5 Shr_s <= 1;
        while ($feof(FileId) == 0) begin
            BitChar = $fgetc(FileId);
            if (BitChar == "1") begin
                Shr_in_s <= 1;
                @(posedge Clk_s);
            end
            else if (BitChar == "0") begin
                Shr_in_s <= 0;
                @(posedge Clk_s);
            end
        end
        $fclose(FileId);
    end
    Shr_s <= 0;
end
endmodule
```

vldd_ch4_ShiftReg32TBFileIO.v

27

Testbench with File Input – 32-Bit Shift Register

- o Test vector file can contain as few or as many test vectors as desired
 - Can add new test vectors and simulate without changing testbench
 - Vectors of "1111111111111111" and "0000000000000000" would match previous testbench for 32-bit shift register
 - Consider simulation only for test vectors "11" and "00"
- o Testbench Simulation
 - Waveform shows simulation for test vectors "11" and "00"
 - Value for Q_s displayed in hexadecimal

 

28

Common Pitfall Unsynthesizable Loop

- Creating an unsynthesizable loop in a description to be synthesized
 - Synthesis must be able to *unroll* the loop into an equivalent straight-line (no loop) sequence of statements
 - To know first statement and last statement of sequence
 - Loop is thus just a shorthand for those statements
 - Index <= 30
 - Anything other than constant may prevent unrolling
 - Index <= Index + 1
 - Anything other than simple index increment/decrement may prevent unrolling
 - Likewise, while loops (even simple ones) may not be unrolled
- For synthesis, best to use only simple *for* loop with constant bounds, and simple index increment/decrement

```

for (Index=0; Index<=30; Index<=Index+1) begin
    R[Index] <= R[Index+1];
end
    
```

↓ Unrolling

```

R[0] <= R[1];
R[1] <= R[2];
...
R[30] <= R[31];
    
```

```


Index = 0;
while (Index <= 30) begin
    ... // loop statements
    Index = Index + 1;
end
    
```

Some tools can unroll this while loop, better to use a for loop

29

4-bit Unsigned/Signed Magnitude Comparator


- Previously
 - Dealt only with unsigned numbers
 - input, output, reg declarations are unsigned unless otherwise specified
- Now consider a simple magnitude comparator that compares a 4-bit unsigned number A with a 4-bit signed number B, with outputs for greater than, less than, and equal
 - A can be 0 to 15 (0000 to 1111)
 - B can be -8 to 7 (1000 to 0111)
 - Need to represent both unsigned and signed numbers

 

30

4-bit Unsigned/Signed Magnitude Comparator

- Declare A input as before, but declare B input with **signed** keyword
- When comparing A and B using "<", first convert unsigned A to signed value using **\$signed** system function
 - "\$signed(A)" would not work – changes positive number to negative
 - e.g., 1000 would change from meaning 8 to meaning -8
 - Instead, first **extend** A to five bits
 - {1'b0,A} – e.g., 1000 becomes 01000
 - Then convert to signed
 - \$signed({1'b0,A}) – e.g., 01000 as 5-bit signed number is still 8 (due to 0 in highest-order bit)
 - Operands of "<" automatically sign-extended to widest operand's width
 - So B extended to 5-bits with sign bit preserved
 - Comparison is thus correct

 

```

`timescale 1 ns/1 ns
module Comp4(A, B, Gt, Eq, Lt);
    input [3:0] A;
    input signed [3:0] B;
    output Gt, Eq, Lt;
    reg Gt, Eq, Lt;


    always @(A, B) begin
        if ($signed({1'b0,A}) < B) begin
            Gt <= 0; Eq <= 0; Lt <= 1;
        end
        else if ($signed({1'b0,A}) > B) begin
            Gt <= 1; Eq <= 0; Lt <= 0;
        end
        else begin
            Gt <= 0; Eq <= 1; Lt <= 0;
        end
    end
end
endmodule
    
```

v1dd_ch4_Comp4.v

31

4-bit Unsigned/Signed Magnitude Comparator

 - Performs comparison using if-else-if construct
 - if A < B:
 - Set Lt to 1, Gt to 0, and Eq to 0
 - If B negative, A will always be greater than B (A is always positive)
 - if (A > B)
 - Gt = 1, Lt = 0, and Eq = 0
 - If A is neither greater or less than
 - Eq = 1, Lt = 0, and Gt = 0



```

`timescale 1 ns/1 ns
module Comp4(A, B, Gt, Eq, Lt);
    input [3:0] A;
    input signed [3:0] B;
    output Gt, Eq, Lt;
    reg Gt, Eq, Lt;

    always @(A, B) begin
        if ($signed({1'b0,A}) < B) begin
            Gt <= 0; Eq <= 0; Lt <= 1;
        end
        else if ($signed({1'b0,A}) > B) begin
            Gt <= 1; Eq <= 0; Lt <= 0;
        end
        else begin
            Gt <= 0; Eq <= 1; Lt <= 0;
        end
    end
end
endmodule
    
```

v1dd_ch4_Comp4.v

32

4-bit Unsigned/Signed Magnitude Comparator

- Testbench should test multiple values for inputs A and B
 - Should perform comparisons for both positive and negative values of B
 - Should have at least one test case in which A is greater than, less than, and equal to B
- Note that reg variable B_s, used to connect with B, defined as **signed**
- Vectors illustrate use of binary constants as well as decimal constants
 - Negative binary constant achieved using 1 in high-order bit (two's complement form)
 - Negative decimal constant requires negative sign "-" in front of constant

```

`timescale 1 ns/1 ns
module Testbench();
  reg [3:0] A_s;
  reg signed [3:0] B_s;
  wire Gt_s, Eq_s, Lt_s;

  Comp4 CompToTest(A_s, B_s, Gt_s, Eq_s, Lt_s);

  initial begin
    A_s <= 4'b0011; B_s <= 4'b0001;
    #10 A_s <= 4'b1111; B_s <= 4'b0111;
    #10 A_s <= 4'b0111; B_s <= 4'b1011;
    #10 A_s <= 4'b0001; B_s <= 4'b0010;
    #10 A_s <= 4'b0001; B_s <= 4'b0001;
    #10 A_s <= 4'b0000; B_s <= 4'b1111;
    #10 A_s <= 4'd1; B_s <= -4'd1;
    #10 A_s <= 4'd1; B_s <= -4'd8;
    // Good testbench needs more vectors
  end
endmodule
    
```

v1dd_ch4_Comp4TB.v

33

4-bit Unsigned/Signed Magnitude Comparator

Simulation

- First two vectors compare positive values for both inputs
 - 0011 > 0001 → Gt_s = 1
 - 1111 > 0111 → Gt_s = 1
- Third test compares A with negative B
 - 0111 > 1011 → Gt_s = 1
 - 7 > -5
- Fourth and fifth test should result in the Lt_s and Eq_s output asserted, respectively
 - 0001 < 0010 → Lt_s = 1
 - 0001 = 0001 → Eq_s = 1
- Next test compares 0 to -1
 - 0000 > 1111 → Gt_s = 1
- Next test compare 1 to -1
- Last test compares 1 to -8

```

`timescale 1 ns/1 ns
module Testbench();
  reg [3:0] A_s;
  reg signed [3:0] B_s;
  wire Gt_s, Eq_s, Lt_s;

  Comp4 CompToTest(A_s, B_s, Gt_s, Eq_s, Lt_s);

  initial begin
    A_s <= 4'b0011; B_s <= 4'b0001;
    #10 A_s <= 4'b1111; B_s <= 4'b0111;
    #10 A_s <= 4'b0111; B_s <= 4'b1011;
    #10 A_s <= 4'b0001; B_s <= 4'b0010;
    #10 A_s <= 4'b0001; B_s <= 4'b0001;
    #10 A_s <= 4'b0000; B_s <= 4'b1111;
    #10 A_s <= 4'd1; B_s <= -4'd1;
    #10 A_s <= 4'd1; B_s <= -4'd8;
    // Good testbench needs more vectors
  end
endmodule
    
```

v1dd_ch4_Comp4TB.v

34

Common Pitfall

- Unintentional use of one of many of Verilog's automatic conversions
 - B_s <= -4'd15
 - 4-bit decimal 15 would be 1111
 - Negative of 1111 (15) is 10001 (-15) – Automatically converted to 5 bits
 - Assignment to B_s drops the high-order bit, making B_s=0001
 - Many similar types of automatic conversions in Verilog
 - Use great caution

```

`timescale 1 ns/1 ns
module Testbench();
  reg [3:0] A_s;
  reg signed [3:0] B_s;
  wire Gt_s, Eq_s, Lt_s;


  Comp4 CompToTest(A_s, B_s, Gt_s, Eq_s, Lt_s);

  initial begin
    ...
    #10 A_s <= 4'd1; B_s <= -4'd1;
    #10 A_s <= 4'd1; B_s <= -4'd15;
    // Good testbench needs more vectors
  end
endmodule
    
```

35

4x32 Register File


- Register Files
 - A register file is more efficient than individual registers if we only need access one or two registers at a time
- Consider 4x32 register file (4 registers, each 32-bits wide)
 - Need decoder with enable
 - Simple extension of Ch 2 decoder
 - Need 32-bit register with parallel load input and a tri-state buffered outputs
 - Implement as 32-bit register with output enable
 - Output of all registers connected to R_data
 - Only one register should output value to bus
 - All other register should output high-impedance
 - Can omit signal-strengthening driver
 - Synthesis tool would determine when/where to insert driver

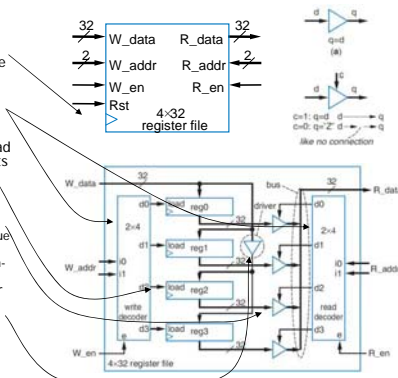

36

32-Bit Register With Output Enable


- High-impedance
 - Represents an output that is neither driven high nor driven low
 - high-impedance \rightarrow written as z or Z
 - " $S \leftarrow z$ "
 - Allows for the outputs of several components to be wired together
 - Only one component should output a 0 or 1
 - All other components should output z
 - Typically achieved using three-state buffers
- Register with Output Enable
 - Three-state buffers are part of register

 

37

32-Bit Register With Output Enable

 - Describing a register with output enable
 - reg variable R used for storage
- Register procedure
 - Resets register to 0s when Rst = 1
 - Stores register value in R when Ld = 1



```

`timescale 1 ns/1 ns
module Reg32wOE(I, Q, Oe, Ld, Clk, Rst);
    input [31:0] I;
    output [31:0] Q;
    reg [31:0] Q;
    input Oe, Ld;
    input Clk, Rst;

    reg [31:0] R;

    // Register Procedure
    always @(posedge Clk) begin
        if (Rst == 1)
            R <= 32'd0;
        else if (Ld == 1)
            R <= I;
        end


    // Output Procedure
    always @(R, Oe) begin
        if (Oe == 1)
            Q <= R;
        else
            Q <= 32'hZZZZZZZ;
        end
    endmodule
    
```

v1dd_ch4_Reg32wOE.v

38

32-Bit Register With Output Enable

 - Output procedure
 - Combinational procedure that controls register output
 - Oe = 1 \rightarrow Output is enabled
 - $Q \leftarrow R$;
 - Oe = 0 \rightarrow Output of register is disabled
 - Output high-impedance
 - $Q \leftarrow 32'hZZZZZZZ$;



```

`timescale 1 ns/1 ns
module Reg32wOE(I, Q, Oe, Ld, Clk, Rst);
    input [31:0] I;
    output [31:0] Q;
    reg [31:0] Q;
    input Oe, Ld;
    input Clk, Rst;

    reg [31:0] R;

    // Register Procedure
    always @(posedge Clk) begin
        if (Rst == 1)
            R <= 32'd0;
        else if (Ld == 1)
            R <= I;
        end


    // Output Procedure
    always @(R, Oe) begin
        if (Oe == 1)
            Q <= R;
        else
            Q <= 32'hZZZZZZZ;
        end
    endmodule
    
```

v1dd_ch4_Reg32wOE.v

39

32-Bit Register With Output Enable

 - Alternative description
 - Replace Output procedure by a single continuous assignment statement (**assign**)
 - Q must be net, not variable
 - Uses conditional operator **? :**
 - A ? B : C
 - If A is true (non-zero), result is B
 - If A is false (zero), result is C
 - Q = Oe ? R : 32'hZZZZZZZ;
 - If Oe is 1, Q gets R
 - If Oe is 0, Q gets 32'hZZZZZZZ



```

`timescale 1 ns/1 ns
module Reg32wOE(I, Q, Oe, Ld, Clk, Rst);
    input [31:0] I;
    output [31:0] Q;
    input Oe, Ld;
    input Clk, Rst;

    reg [31:0] R;

    // Register Procedure
    always @(posedge Clk) begin
        if (Rst == 1)
            R <= 32'd0;
        else if (Ld == 1)
            R <= I;
        end

    assign Q = Oe ? R : 32'hZZZZZZZ;
endmodule
    
```

Same behavior as previous description, just more compact

v1dd_ch4_Reg32wOEcond.v

40

32-Bit Register With Output Enable

Testbench

- Reset register and enable output →
Oe_s <= 1;
- Load register with value
32'h000000FF
 - Use self-check to verify correctness
- New operator use
 - !=
 - Does bit-by-bit comparison
 - Handles z and x values
 - ===
 - For bit-by-bit equality check
 - Handles z and x values
 - == and != don't handle z or x
 - Returns x (unknown) if z or x present in either operand
 - != and === never return x
- Oe_s <= 0; → Disable output
 - Use self-check to verify that output is high-impedance

```

... // Vector Procedure
initial begin
    Rst_s <= 1;
    Oe_s <= 1; Ld_s <= 0;
    I_s <= 32'h00000000;
    @(posedge Clk_s);
    #5 Rst_s <= 0;
    @(posedge Clk_s);
    #5 Ld_s <= 1; I_s <= 32'h000000FF;
    @(posedge Clk_s);
    #5;
    if (Q_s != 32'h000000FF)
        $display("Failed output enabled");
    Ld_s <= 0; Oe_s <= 0;
    #5;
    if (Q_s != 32'hZZZZZZZZ)
        $display("Failed output disabled");
end
...
    
```

v1dd_ch4_Reg32wOEB.v

41

Structural 4x32 Register File

Register File

- Structurally connect decoders and registers to create register file

```

`timescale 1 ns/1 ns
module RegFile4x32(R_Addr,W_Addr,R_en,W_en,R_Data,W_Data,Clk,Rst);
    input [1:0] R_Addr, W_Addr;
    input R_en, W_en;
    output [31:0] R_Data;
    input [31:0] W_Data;
    input Clk, Rst;

    wire W_d3, W_d2, W_d1, W_d0;
    wire R_d3, R_d2, R_d1, R_d0;

    Dcd2x4wEn R_Dcd (R_Addr[1],R_Addr[0],R_en,
                    R_d3,R_d2,R_d1,R_d0);
    Dcd2x4wEn W_Dcd (W_Addr[1],W_Addr[0],W_en,
                    W_d3,W_d2,W_d1,W_d0);

    Reg32wOE Reg0 (W_Data,R_Data,R_d0,W_d0,Clk,Rst);
    Reg32wOE Reg1 (W_Data,R_Data,R_d1,W_d1,Clk,Rst);
    Reg32wOE Reg2 (W_Data,R_Data,R_d2,W_d2,Clk,Rst);
    Reg32wOE Reg3 (W_Data,R_Data,R_d3,W_d3,Clk,Rst);
endmodule
    
```

v1dd_ch4_RegFile4x32Struct.v

42

Multiple Drivers for One Net

- Earlier examples all had exactly one driver per net
- But structural register file has four drivers for net R_data
 - One from each Reg32wOE instantiation
- Resolving multiple driven values into one value done as follows
 - 0 and z → 0
 - 1 and z → 1
 - z and z → z
 - 0 and 1 → x
 - Note: Other resolutions also defined, such as 0 and 1 → x, 0 and 0 → 0, 1 and 1 → 1, but we should not allow those situations to happen

```

`timescale 1 ns/1 ns // Vector Procedure
initial begin
    Rst_s <= 1;
    R_Addr_s <= 0'b00; W_Addr_s <= 0'b00;
    R_en_s <= 0; W_en_s <= 0;
    @(posedge Clk_s);
    #5 Rst_s <= 0;
    @(posedge Clk_s);
    #5;
    // Write values to registers
    for (Index=0; Index<=3; Index=Index+1) begin
        W_Addr_s <= Index; W_Data_s <= Index;
        W_en_s <= 1;
        @(posedge Clk_s);
        #5;
    end
    W_en_s <= 0;
    // Check for correct read values from registers
    for (Index=0; Index<=3; Index=Index+1) begin
        R_Addr_s <= Index; R_en_s <= 1;
        @(posedge Clk_s);
        #5;
        if (R_Data_s != Index)
            $display("Failed case %d.", Index);
    end
    R_en_s <= 0;
    #5;
    if (R_Data_s != 32'hZZZZZZZZ)
        $display("Failed no read case.");
end
    
```

- Writes some values, then reads and checks

v1dd_ch4_RegFile4x32TB.v

44

43

Behavioral 4x32 Register File

- Register File
 - Can define behaviorally
- Declares a 4-element array
 - Each element 32-bits
 - Element address range defines starting and ending addresses for array elements
 - Specified at end of declaration to distinguish from vector range specification
 - Array elements accessed using index
 - RegFile[0] <= 32'd0; – sets first array element to 32 0s
 - Note that vector may be used as array index: RegFile[W_Addr]

```

`timescale 1 ns/1 ns
module RegFile4x32(R_Addr, W_Addr, R_en, W_en,
                  R_Data, W_Data, Clk, Rst);
    input [1:0] R_Addr, W_Addr;
    input R_en, W_en;
    output reg [31:0] R_Data;
    input [31:0] W_Data;
    input Clk, Rst;

    reg [31:0] RegFile [0:3];

    // Write procedure
    always @(posedge Clk) begin
        if (Rst==1) begin
            RegFile[0] <= 32'd0;
            RegFile[1] <= 32'd0;
            RegFile[2] <= 32'd0;
            RegFile[3] <= 32'd0;
        end
        else if (W_en==1) begin
            RegFile[W_Addr] <= W_Data;
        end
    end

    // Read procedure
    always @* begin
        if (R_en==1)
            R_Data <= RegFile[R_Addr];
        else
            R_Data <= 32'hZZZZZZZZ;
        end
    end
endmodule
vidd_ch4_RegFile4x32Beh.v
    
```

45

Behavioral 4x32 Register File

- Note: Must use earlier-described implicit sensitivity list "@*" for Read procedure
 - Because event control may not include an array
 - Could instead include each array element in list (RegFile[0], RegFile[1], ...), but cumbersome, especially for large arrays

```

`timescale 1 ns/1 ns
module RegFile4x32(R_Addr, W_Addr, R_en, W_en,
                  R_Data, W_Data, Clk, Rst);
    input [1:0] R_Addr, W_Addr;
    input R_en, W_en;
    output reg [31:0] R_Data;
    input [31:0] W_Data;
    input Clk, Rst;

    reg [31:0] RegFile [0:3];

    // Write procedure
    always @(posedge Clk) begin
        if (Rst==1) begin
            RegFile[0] <= 32'd0;
            RegFile[1] <= 32'd0;
            RegFile[2] <= 32'd0;
            RegFile[3] <= 32'd0;
        end
        else if (W_en==1) begin
            RegFile[W_Addr] <= W_Data;
        end
    end

    // Read procedure
    always @* begin
        if (R_en==1)
            R_Data <= RegFile[R_Addr];
        else
            R_Data <= 32'hZZZZZZZZ;
        end
    end
endmodule
vidd_ch4_RegFile4x32Beh.v
    
```

46

Common Pitfall Using logical operators instead of bitwise

- Both bitwise and logical AND, OR, and NOT operators exist
 - Easy to mistakenly use logical operator instead bitwise operator, and vice versa
 - May work for single bit inputs, but will produce incorrect results for multi-bit vectors
 - Bitwise Operators:
 - &: bitwise AND
 - |: bitwise OR
 - ~: bitwise NOT
 - Performs operation bit-by-bit resulting in multi-bit vector as wide as largest input operand
 - Logical Operators:
 - &&: logical AND
 - ||: logical OR
 - !: logical NOT (negation)
 - Performs operation by interpreting input operands as logical values of true or false, resulting in a single bit output of 0 or 1

```

if( A & 4'b0100 ) begin
    BitSet <= 1;
end
else begin
    BitSet <= 0;
end

    Bitwise & operator results
    in correct output

if( A && 4'b0100 ) begin
    BitSet <= 1;
end
else begin
    BitSet <= 0;
end

    Logical && operator
    results in incorrect output
    
```

47

Common Pitfall Using logical operators instead of bitwise

- Consider a simple if-else statement that will determine if bit 2 of a 4-bit input A is 1, and set an output BitSet accordingly
 - Using the bitwise & operator will result in correct output
 - Assume A is 1000: 1000 & 0100 results in 0000
 - 1&0=0, 0&1=0, 0&0=0, and 0&0=0
 - Within an if expression, a value of zero is considered false and BitSet will be assigned the correct value of 0 within else part
 - Using the logical && operator will result in incorrect output
 - Assume A is 1000: 1000 && 0100 results in 1 – both inputs are non-zero and will be interpreted as true (1), where 1&&1=1
 - Within if expression, 1 is considered true and BitSet will be assigned the incorrect value of 1 within if part

```

if( A & 4'b0100 ) begin
    BitSet <= 1;
end
else begin
    BitSet <= 0;
end

    Bitwise & operator results
    in correct output

if( A && 4'b0100 ) begin
    BitSet <= 1;
end
else begin
    BitSet <= 0;
end

    Logical && operator
    results in incorrect output
    
```

48