

ECE 274 Digital Logic

Datapath Components – Subtractors, Two’s Complement, Overflow, ALUs, Register Files


Digital Design 4.8 – 4.10



Digital Design

Chapter 4: Datapath Components

 Slides to accompany the textbook *Digital Design*, First Edition, by Frank Vahid, John Wiley and Sons Publishers, 2007. <http://www.dvvhid.com>





Copyright © 2007 Frank Vahid

Instructors of courses requiring Vahid's Digital Design textbook (published by John Wiley and Sons) have permission to modify and use these slides for customary course-related activities, subject to keeping this copyright notice in place and unmodified. These slides may be posted as ~~unmodified~~ pdf versions on publicly-accessible course websites. PowerPoint source for pdf with animations may ~~not~~ be posted to publicly-accessible websites, but may be posted for students on internal protected sites or distributed directly to students by other electronic means. Instructors may make printouts of the slides available to students for a reasonable photocopying charge, without incurring royalties. Any other use requires explicit permission. Instructors may obtain PowerPoint source or obtain special use permissions from Wiley – see <http://www.dvvhid.com> for information.

Datapath Components Subtractor

- Can build subtractor as we built carry-ripple adder
 - Mimic subtraction by hand
 - Compute borrows from columns on left

- Use full-subtractor component:

  

Datapath Components

Subtractor Example: Color Space Converter – RGB to CMY

- Color
 - Often represented as weights of three colors: red, green, and blue (RGB)
 - Perhaps 8 bits each, so specific color is 24 bits
 - White: R=11111111, G=11111111, B=11111111
 - Black: R=00000000, G=00000000, B=00000000
 - Other colors: values in between, e.g., R=00111111, G=00000000, B=00001111 would be a reddish purple
 - Good for computer monitors, which mix red, green, and blue lights to form all colors




- Printers use opposite color scheme
 - Because inks *absorb* light
 - Use complementary colors of RGB: Cyan (absorbs red), reflects green and blue, Magenta (absorbs green), and Yellow (absorbs blue)

Datapath Components

Subtractor Example: Color Space Converter – RGB to CMY

 - Printers must quickly convert RGB to CMY
 - $C=255-R$, $M=255-G$, $Y=255-B$
 - Use subtractors as shown



5

Datapath Components

Subtractor Example: Color Space Converter – RGB to CMYK

- Try to save colored inks
 - Expensive
 - Imperfect – mixing C, M, Y doesn't yield good-looking black
- Solution: Factor out the black or gray from the color, print that part using black ink
 - e.g., CMY of $(250,200,200) = (200,200,200) + (50,0,0)$.
 - $(200,200,200)$ is a dark gray – use black ink




6

Datapath Components

Subtractor Example: Color Space Converter – RGB to CMYK

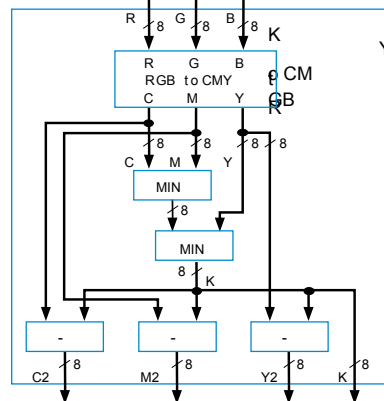- Call black part K
 - $(200,200,200)$: $K=200$
 - (Letter "B" already used for blue)
- Compute minimum of C, M, Y values
 - Use MIN component designed earlier, using comparator and mux, to compute K
 - Output resulting K value, and subtract K value from C, M, and Y values
 - Ex: Input of $(250,200,200)$ yields output of $(50,0,0,200)$



7


Representing Negative Numbers: Two's Complement

- Negative numbers common
 - How represent in binary?
- Signed-magnitude
 - Use leftmost bit for sign bit
 - So -5 would be:
 - 1101 using four bits
 - 10000101 using eight bits
- Better way: Two's complement
 - Big advantage: Allows us to perform subtraction using addition
 - Thus, only need adder component, no need for separate subtractor component!

8

Ten's Complement

 - Before introducing two's complement, let's consider ten's complement
 - Complements for each base ten number shown to right – Complement is the number that when added results in 10
- Nice feature of ten's complement
 - Instead of subtracting a number, adding its complement results in answer exactly 10 too much
 - So just drop the 1 – results in subtracting using addition only




Two's Complement is Easy to Compute: Just Invert Bits and Add 1

- Hold on!
 - Sure, adding the ten's complement achieves subtraction using addition only
 - But don't we have to perform *subtraction* to determine the complement in the first place?
 - True – but in binary, two's complement can be computed **easily**
 - Two's complement of 011 is 101, because $011 + 101 = 1000$
 - Could compute complement of 011 as $1000 - 011 = 101$
 - Easier method: Just invert all the bits, and add 1**
 - The complement of 011 is $100+1 = 101$ -- it works!

10

Datapath Components Two's Complement

 
- What is the 4-bit binary two's complement representation for the decimal number -5?
 - 0101
 - 1101
 - 1010
 - 1011



11

Datapath Components Two's Complement

 - What is the 5-bit binary two's complement representation for the decimal number -5?
 - 00101
 - 10101
 - 10011
 - 11011




12

Datapath Components

Two's Complement

 - How many bits are needed to represent the number -12 in binary?
 - 3
 - 4
 - 5
 - Impossible!




13

Datapath Components

Two's Complement

 - What is the 5-bit binary two's complement representation for the decimal number 7?
 - 00111
 - 10111
 - 11001
 - Two's complement can only represent negative numbers




14

Datapath Components

Two's Complement

 - What is the decimal equivalent of the two's complement binary number 111?
 - 1
 - 7
 - 1
 - 3




15

Datapath Components

Two's Complement

 - What is the decimal equivalent of the two's complement binary number 1000?
 - 0
 - 1
 - 8
 - 8




16

Datapath Components

Two's Complement

 - What is the decimal equivalent the two's complement binary number 0101?
 - 5
 - 5
 - 11
 - Nothing




17

Datapath Components

Two's Complement

 - What is the decimal equivalent the two's complement binary number 111111111111?
 - 1
 - 1
 - Who cares?
 - I don't know!



18

Datapath Components


Two's Complement Subtractor Built with an Adder

- Using two's complement

$$A - B = A + (-B)$$

$$= A + (\text{two's complement of } B)$$
 
$$= A + \text{invert_bits}(B) + 1$$
- So build subtractor using adder by inverting B's bits, and setting carry in to 1




19

Datapath Components

Adder/Subtractor

 - Adder/subtractor: control input determines whether add or subtract
 - Can use 2x1 mux – sub input passes either B or inverted B
 - Alternatively, can use XOR gates – if sub input is 0, B's bits pass through; if sub input is 1, XORs invert B's bits



20

Datapath Components

Overflow

- Sometimes result can't be represented with given number of bits
 - Either too large magnitude of positive or negative
 - e.g., 4-bit two's complement addition of 0111+0001 (7+1=8). But 4-bit two's complement can't represent number >7
 - 0111+0001 = 1000 WRONG answer, 1000 in two's complement is -8, not +8
 - Adder/subtractor should indicate when overflow has occurred, so result can be discarded

21

Datapath Components

Overflow: Detecting Overflow: Method 1

- Assuming 4-bit two's complement numbers, can detect overflow by detecting when the two numbers' sign bits are the same but are different from the result's sign bit
 - If the two numbers' sign bits are different, overflow is impossible
 - Adding a positive and negative can't exceed largest magnitude positive or negative
- Simple circuit
 - overflow = $a_3'b_3's_3 + a_3'b_3s_3'$
 - Include "overflow" output bit on adder/subtractor

sign bits		
0 1 1 1 + 0 0 0 1 ----- 1 0 0 0 overflow (a)	1 1 1 1 + 1 0 0 0 ----- 0 1 1 1 overflow (b)	1 0 0 0 + 0 1 1 1 ----- 1 1 1 1 no overflow (c)

If the numbers' sign bits have the same value, which differs from the result's sign bit, overflow has occurred.

22

Datapath Components

Overflow: Detecting Overflow: Method 2

- Even simpler method: Detect difference between carry-in to sign bit and carry-out from sign bit
- Yields simpler circuit: overflow = $c_3 \text{ xor } c_4$

1 1 1 0 1 1 1 + 0 0 0 1 ----- 0 1 0 0 0 overflow (a)	0 0 0 1 1 1 1 + 1 0 0 0 ----- 1 0 1 1 1 overflow (b)	0 0 0 1 0 0 0 + 0 1 1 1 ----- 0 1 1 1 1 no overflow (c)
--	--	---

If the carry into the sign bit column differs from the carry out of that column, overflow has occurred.

23

Datapath Components

Magnitude Comparator Example: Minimum of Two Numbers

- Design a combinational component that computes the minimum of two 8-bit signed numbers

24

Datapath Components

Arithmetic-Logic Unit (ALU)

ALU

- Component that can perform any of various arithmetic (add, subtract, increment, etc.) and logic (AND, OR, etc.) operations, based on control inputs

Motivation:

- Suppose want multi-function calculator that not only adds and subtracts, but also increments, ANDs, ORs, XORs, etc.

TABLE 4.2 Desired calculator operations

Inputs			Operation	Sample output if A=00001111, B=00000101
x	y	z		
0	0	0	$S = A + B$	S=00010100
0	0	1	$S = A - B$	S=00001010
0	1	0	$S = A + 1$	S=00010000
0	1	1	$S = A$	S=00001111
1	0	0	$S = A \text{ AND } B$ (bitwise AND)	S=00000101
1	0	1	$S = A \text{ OR } B$ (bitwise OR)	S=00001111
1	1	0	$S = A \text{ XOR } B$ (bitwise XOR)	S=00001010
1	1	1	$S = \text{NOT } A$ (bitwise complement)	S=11100000


25

Datapath Components

Arithmetic-Logic Unit (ALU)

More efficient design uses ALU

 - ALU design not just separate components multiplexed (same problem as previous slide!),
- Instead, ALU design uses single adder, plus logic in front of adder's A and B inputs
 - Logic in front is called an arithmetic-logic extender
- Extender modifies the A and B inputs such that desired operation will appear at output of the adder




26

Datapath Components

Arithmetic-Logic Extender in Front of ALU

TABLE 4.2 Desired calculator operations

Inputs			Operation	Sample output if A=00001111, B=00000101
x	y	z		
0	0	0	$S = A + B$	S=00010100
0	0	1	$S = A - B$	S=00001010
0	1	0	$S = A + 1$	S=00010000
0	1	1	$S = A$	S=00001111
1	0	0	$S = A \text{ AND } B$ (bitwise AND)	S=00000101
1	0	1	$S = A \text{ OR } B$ (bitwise OR)	S=00001111
1	1	0	$S = A \text{ XOR } B$ (bitwise XOR)	S=00001010
1	1	1	$S = \text{NOT } A$ (bitwise complement)	S=11100000

 

- xyz=000: Want $S=A+B$ – just pass a to ia, b to ib, and set cin=0
- xyz=001: Want $S=A-B$ – pass a to ia, b' to ib, and set cin=1
- xyz=010: Want $S=A+1$ – pass a to ia, set ib=0, and set cin=1
- xyz=011: Want $S=A$ – pass a to ia, set ib=0, and set cin=0
- xyz=1000: Want $S=A \text{ AND } B$ – set ia=a*b, b=0, and cin=0
- others: likewise
- Based on above, create logic for ia(x,y,z,a,b) and ib(x,y,z,a,b) for each abext, and create logic for cin(x,y,z), to complete design of the AL-extender component


27

Datapath Components

Register Files

MxN Register File

 - Provides efficient access to M N-bit-wide registers
- If we have many registers but only need access one or two at a time, a register file is more efficient
- Ex: Above-mirror display (earlier example), but this time having 16 32-bit registers
 - Too many wires, and big mux is too slow




28

Datapath Components

Register Files

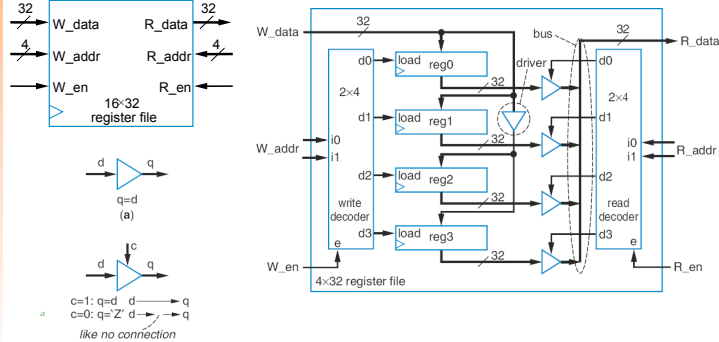- Instead, want component that has one data input and one data output, and allows us to specify which internal register to write and which to read




29

Datapath Components

Register Files: Timing Diagram

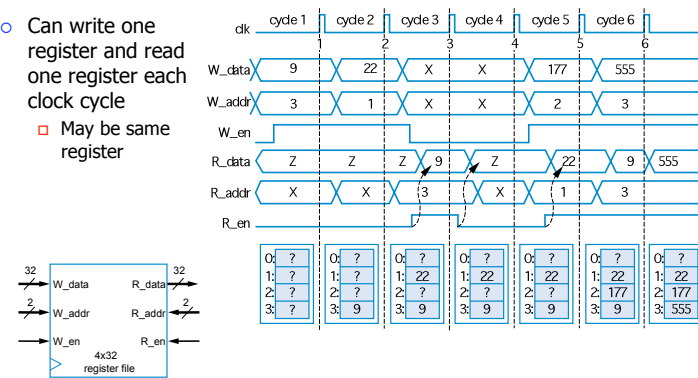- Can write one register and read one register each clock cycle
 - May be same register



30