

# ECE 274 Digital Logic – Spring 2009

## Combinational Logic Design Process and Common Combinational Components


*Digital Design 2.7 – 2.10*



# Digital Design
 
## Chapter 2: Combinational Logic Design

Slides to accompany the textbook *Digital Design*, First Edition,  
by Frank Vahid, John Wiley and Sons Publishers, 2007.  
<http://www.ddvahid.com>



Copyright © 2007 Frank Vahid

Instructors of courses requiring Vahid's Digital Design textbook (published by John Wiley and Sons) have permission to modify and use these slides for customary course-related activities, subject to keeping this copyright notice in place and unmodified. These slides may be posted as [unannotated pdf](#) versions on publicly-accessible course websites. PowerPoint source (or pdf with animations) may [not](#) be posted to publicly-accessible websites, but may be posted for students on internal protected sites or distributed directly to students by other electronic means. Instructors may make printouts of the slides available to students for a reasonable photocopying charge, without incurring royalties. Any other use requires explicit permission. Instructors may obtain PowerPoint source or obtain special use permissions from Wiley – see <http://www.dfvahid.com> for information.

2

## Digital Logic – Combinational Logic

*Combinational Logic Design Process*

2.7


Step	Description
Step 1 <b>Capture</b> the function	Create a truth table or equations, <b>whichever is most natural for the given problem</b> , to describe the desired behavior of the combinational logic.
Step 2 <b>Convert</b> to equations	This step is only necessary if you captured the function using a truth table instead of equations. Create an equation for each output by ORing all the minterms for that output. Simplify the equations if desired.
Step 3 <b>Implement</b> as a gate-based circuit	For each output, create a circuit corresponding to the output's equation. (Sharing gates among multiple outputs is OK optionally.)

3

## Digital Logic – Combinational Logic

*Combinational Logic Design Process Example: Three 1s Detector*

 - Problem: Detect three consecutive 1s in 8-bit input: abcdefgh
  - 00011101 → 1    10101011 → 0
  - 11110000 → 1
- Step 1: Capture** the function
  - Truth table or equation?
    - Truth table too big;  $2^8=256$  rows
    - Equation: create terms for each possible case of three consecutive 1s
  - $y = abc + bcd + cde + def + efg + fgh$
- Step 2: Convert** to equation -- already done
- Step 3: Implement** as a gate-based circuit



4

## Digital Logic – Combinational Logic

Combinational Logic Design Process Example: Number of 1s Count

- Problem: Output in binary on two outputs yz in the number of 1s on three inputs

- 010 → 01 101 → 10 000 → 00

- Step 1: Capture** the function


- Truth table or equation?
  - Truth table is straightforward

- Step 2: Convert** to equation

- $y = a'bc + ab'c + abc' + abc$
- $z = a'b'c + a'bc' + ab'c' + abc$

- Step 3: Implement** as a gate-based circuit

Inputs			# of 1s	Outputs	
a	b	c		y	z
0	0	0	(0)	0	0
0	0	1	(1)	0	1
0	1	0	(1)	0	1
0	1	1	(2)	1	0
1	0	0	(1)	0	1
1	0	1	(2)	1	0
1	1	0	(2)	1	0
1	1	1	(3)	1	1

 


5

## Digital Logic – Combinational Logic

2.8

More Gates

 

- NAND: Opposite of AND (“NOT AND”)
  - NAND same as AND with power & ground switched
    - Why? nMOS conducts 0s well, but not 1s (reasons beyond our scope) -- so NAND more efficient
- NOR: Opposite of OR (“NOT OR”)
  - Likewise, NOR same as OR with power/ground switched
- XOR: Exactly 1 input is 1, for 2-input XOR. (For more inputs -- odd number of 1s)
  - AND in CMOS: NAND with NOT
- XNOR: Opposite of XOR (“NOT XOR”)
  - OR in CMOS: NOR with NOT
  - So NAND/NOR more common

6


## Digital Logic – Combinational Logic

Completeness of NAND

- Any Boolean function can be implemented *using just NAND gates*. Why?

- Need AND, OR, and NOT
- NOT: 1-input NAND (or 2-input NAND with inputs tied together)
- AND: NAND followed by NOT
- OR: NAND preceded by NOTs

- Likewise for NOR

 

7

## Digital Logic – Combinational Logic

Number of Possible Boolean Functions

- How many possible functions of 2 variables?
  - 2<sup>2</sup> rows in truth table, 2 choices for each
  - 2<sup>(2<sup>2</sup>)</sup> = 2<sup>4</sup> = 16 possible functions
- N variables
  - 2<sup>N</sup> rows
  - 2<sup>(2<sup>N</sup>)</sup> possible functions

a	b	F
0	0	0 or 1 2 choices
0	1	0 or 1 2 choices
1	0	0 or 1 2 choices
1	1	0 or 1 2 choices

2<sup>4</sup> = 16 possible functions

a	b	f0	f1	f2	f3	f4	f5	f6	f7	f8	f9	f10	f11	f12	f13	f14	f15
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
	0	a AND b		a		b		a XOR b		a OR b		a NOR b		a XNOR b		b	
																a	
																a NAND b	
																1	

8

## Digital Logic – Combinational Logic

### Decoders and Muxes

2.9

- Decoder: Popular combinational logic building block, in addition to logic gates

- Converts input binary number to one high output

- 2-input decoder: four possible input binary numbers

- So has four outputs, one for each possible input binary number


- Internal design

- AND gate for each output to detect input combination

- Decoder with enable e

- Outputs all 0 if e=0
- Regular behavior if e=1

- n-input decoder:  $2^n$  outputs

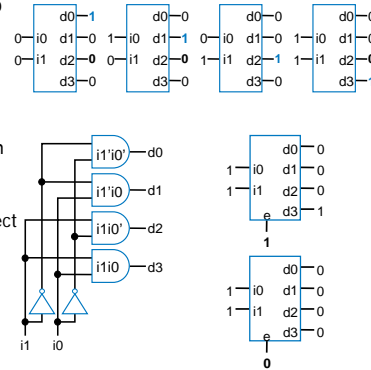



9

## Digital Logic – Combinational Logic
  
### N-bit Mux

- What output of a 3x8 decoder will be asserted if  $i_2i_1i_0 = 110$ ?

- $d_0 = 1$
- $d_3 = 1$
- $d_6 = 1$
- $d_7 = 1$



10

## Digital Logic – Combinational Logic


### Multiplexor (Mux)

- Mux: Another popular combinational building block

- Routes one of its N data inputs to its one output, based on binary value of select inputs

- 4 input mux  $\rightarrow$  needs 2 select inputs to indicate which input to route through
- 8 input mux  $\rightarrow$  3 select inputs
- N inputs  $\rightarrow \log_2(N)$  selects


- Like a railyard switch

 


11

## Digital Logic – Combinational Logic

### Mux Internal Design

 

2x1 mux

 


4x1 mux

12

## Digital Logic – Combinational Logic
 
### Mux Example

- City mayor (*with no budget for good voting system*) can set four switches up or down, representing his/her vote on each of four proposals, numbered 0, 1, 2, 3
- City manager can display any such vote on large green/red LED (light) by setting two switches to represent binary 0, 1, 2, or 3
- Use 4x1 mux




13

## Digital Logic – Combinational Logic

### N-bit Mux

 - Example: Two 4-bit inputs, A ( $a_3 a_2 a_1 a_0$ ), and B ( $b_3 b_2 b_1 b_0$ )
  - 4-bit 2x1 mux (just four 2x1 muxes sharing a select line) can select between A or B





14

## Digital Logic – Combinational Logic

### N-bit Mux

- If  $A=5$ ,  $B=2$ , what is the output of the 4-bit 2x1 mux if  $s_0 = 1$ ?


- 0
- 5
- 2
- 7

  

15

## Digital Logic – Combinational Logic

### N-bit Mux Example

 


- Four possible display items
  - Temperature (T), Average miles-per-gallon (A), Instantaneous mpg (I), and Miles remaining (M) -- each is 8-bits wide
  - Choose which to display using two inputs x and y
  - Use 8-bit 4x1 mux

16
 
## Digital Logic – Combinational Logic

*Non-Ideal Gate Behavior -- Delay*

- Real gates have some delay
  - Outputs don't change immediately after inputs change




17
 
## Digital Logic – Combinational Logic

*Encoders*

- Encoder:** Combinational logic building block with opposite functionality of decoder
  - Outputs binary encoding for input signal that is 1
  - 4x2 encoder would have four inputs and 2 outputs



- What if two inputs are 1?
  - Can use a **priority encoder**
  - Gives priority to the highest input that is 1, and outputs binary encoding for that input
  - Example: If  $d3=1$  and  $d1=1$ , will output  $e0=1$  and  $e1=1$  because  $d3$  has priority



18

## Digital Logic – Combinational Logic

*In Class Exercise*

- Design a 4x2 encoder using AND, OR, and NOT gates.

19