

# ECE 372 – Microcontroller Design

## Digital IO Ports



# ECE 372 – Microcontroller Design

## Digital IO Ports

- Digital IO Ports
  - *E.g. Port A, Port B*
  - Used to interface with many devices
    - Switches
    - LEDs
    - LCD
    - Keypads
    - Relays
    - Stepper Motors
  - Interface with digital IO requires us to connect the devices correctly and write code to interface with the devices

## ECE 372 – Microcontroller Design

### Digital IO Ports

- PIC24F – *Where can we connect external hardware?*
  - Unused ports (most ports has digital IO functionality)
  - Expand through the serial interface
    - SPI serial peripheral interface
    - UART
    - I<sup>2</sup>C
  - External Components to Expand IO Ports

## ECE 372 – Microcontroller Design

### Digital IO Ports


- PIC24F – *Where can we connect external hardware?*
  - 16-bit 28-pin Starter Board
    - Port B (RB0 – RB15)
    - Port A (RA0, RA1, RA4)
    - RB0, RB1, RB4, and RA4 can only be used on stand-alone programming
      - Corresponds to pins 3, 4, 11, and 12

## ECE 372 – Microcontroller Design

### Digital IO Ports

- Digital Inputs

- What does the following circuit do?

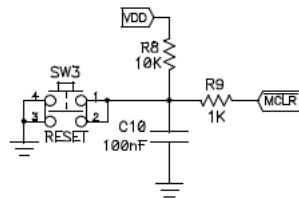


*MCLR (Reset) Switch Schematic from 16-bit 28-pin Starter Board*

- Note:  $\overline{\text{MCLR}}$  is an active low signal.
  - Active low signals are **asserted** if the input is low (0)
  - For PICs, if the MCLR input is 0 the PIC is reset

## ECE 372 – Microcontroller Design
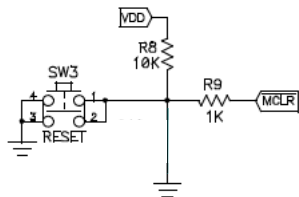
### Digital IO Ports

- Used for Hardware De-Bouncing of Switch Input




- Resistor connected to Vdd is used to **Pull-Up** the input pin to a logical high
  - Vdd is 3.3V for PIC24F
  - Logic high (1) will be seen when button is not pressed
  - Logic high (1) will be seen when button is not pressed
    - Pressing switch creates conduction path to ground
- Without capacitor, simple switches exhibit bouncing

## ECE 372 – Microcontroller Design

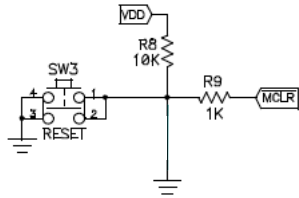
### Digital IO Ports

- Used for Hardware De-Bouncing of Switch Input



Analog Voltage at Input Pin:


Digital Value Read by PIC:

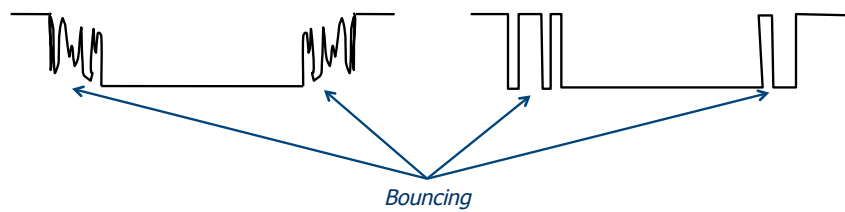

## ECE 372 – Microcontroller Design

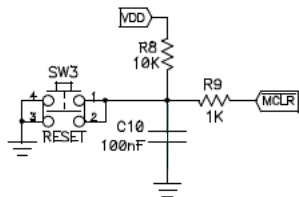
### Digital IO Ports

- Charging and discharging of capacitor reduces bouncing behavior



Analog Voltage at Input Pin:


Digital Value Read by PIC:

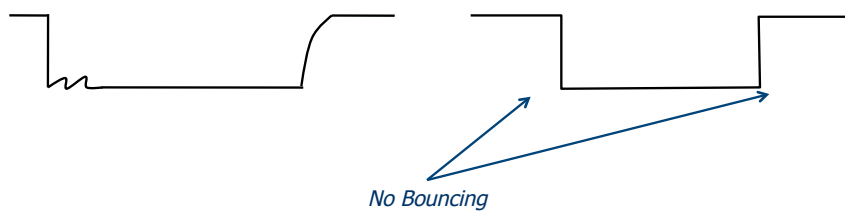

## ECE 372 – Microcontroller Design
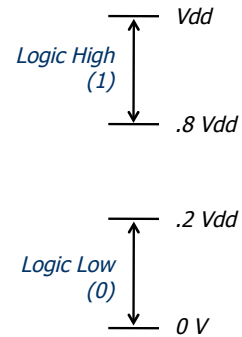
### Digital IO Ports

- When is a digital input a logic high (1) versus logic low (0)
  - Depends on voltage standard used by the digital device
  - Lots of standards exist
- PIC24F
  - Logic Low Input:  $< 0.2 V_{dd}$  (0.66V)
  - Logic High Input:  $> 0.8 V_{dd}$  (2.64V)
  - What about between 0.2 and .8 Vdd?
    - All digital inputs have Schmitt Triggers




## ECE 372 – Microcontroller Design


### Digital IO Ports

- Schmitt Trigger
  - Removes hysteresis between transition from low to high and high to low
  - Helps in de-bouncing digital inputs (*but does not solve it on its own*)

Analog Voltage at Input Pin:

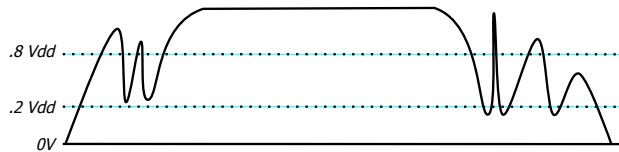

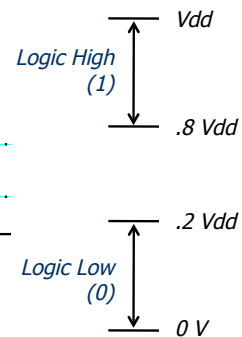Digital Value Read by PIC with Schmitt Trigger:



## ECE 372 – Microcontroller Design

### Digital IO Ports

- Software De-bouncing

- De-bouncing can be done in software using timed waits
- Simplifies external hardware needs
- Pseudocode for software de-bounce for button press

```
// wait for button press
while (switch == 1);

// delay for 5 to 10 ms
for (i=0; i<SOME_LARGER_NUMBER; i++);
```


- Bad example of software de-bounce as timing using for loops is imprecise.
  - Is there a better way?

## ECE 372 – Microcontroller Design
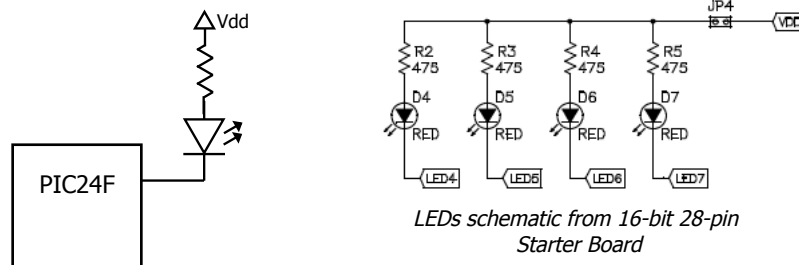
### Digital IO Ports

- Directly Controlling LEDs


- PIC24F can directly control LED from output ports
  - Write 0 to port: Turns LED on
  - Write 1 to port: Turns LED off



## ECE 372 – Microcontroller Design
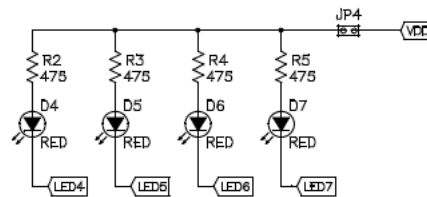
### Digital IO Ports

- Directly Controlling LEDs
  - How much current is drawn by IO?
    - $I = V / R = 3.3 / 475 = 6.9 \text{ mA}$
  - How much current can be drawn by the PIC's IO pin?
    - Check the datasheet
    - 25 mA for PIC24F
  - How much current can be drawn by **ALL** IO pins of the PIC?
    - Check the datasheet
    - 200 mA



LEDs schematic from 16-bit 28-pin Starter Board

## ECE 372 – Microcontroller Design


### Digital IO Ports

- Configure IO Pins for PIC24F
  - Each IO Port has at least three registers
    - TRIS : Controls tri-state driver for direction (1 -> Input, 0 -> Output)
    - LAT : Output latch for writing value to the port (or reading current value assigned to port)
    - PORT : Value read directly from the port
  - Additional Registers Needed for Some IOs
    - CNPU : Enables weak internal pull-up resistor
    - AD1PCFG : Configures ports as analog or digital
    - ODC : Enables open drain collector configuration

## ECE 372 – Microcontroller Design
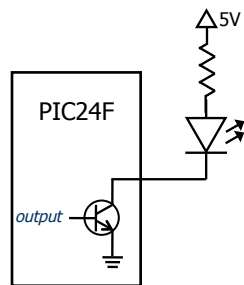
### Digital IO Ports

- Directly Controlling LEDs
  - What if we need to control a 5V digital output?
    - Can use the Open-Drain Collector configuration for the digital outputs
    - ODC registers control configuration (1 -> open drain configuration)




- Use NPN transistor as digital switch
  - NPN in On if base is high (1)
  - Still limited to current limit of digital IO pin

## ECE 372 – Microcontroller Design
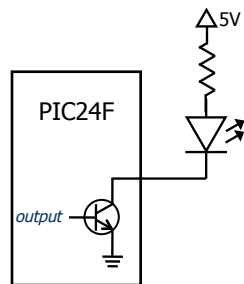
### Digital IO Ports

- Directly Controlling LEDs
  - Brightness of LED can be controlled by controlling the current
  - LEDs also have maximum current draw (exceeding this will destroy the LED)
  - Using open collector, what is the smallest value resistor can we use:
    - $R = 5V / 25 \text{ mA} = 200 \Omega$
    - With  $330 \Omega$  :  $I = 5V / 330 \Omega = 15 \text{ mA}$






## ECE 372 – Microcontroller Design
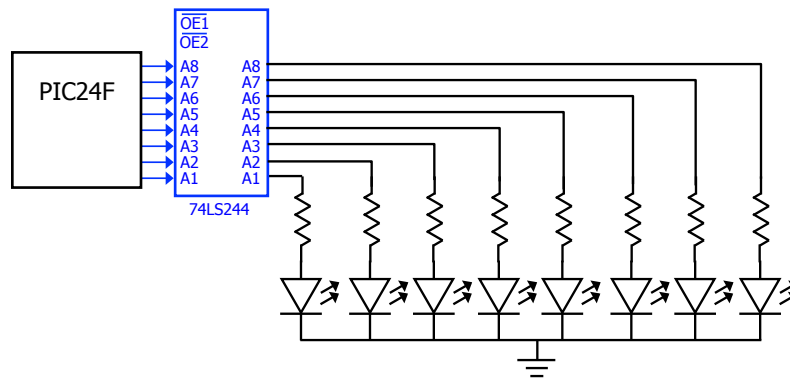
### Digital IO Ports


- Directly Controlling LEDs
  - We can use external IC to drive the LEDs
    - Reduce current driven by microcontroller and protects it
  - 74LS244IC Tri-state Buffer/Line Driver/Line Receiver
    - Used to provide power for LEDs
    - Has OE signals that can be used to disable the output



## ECE 372 – Microcontroller Design
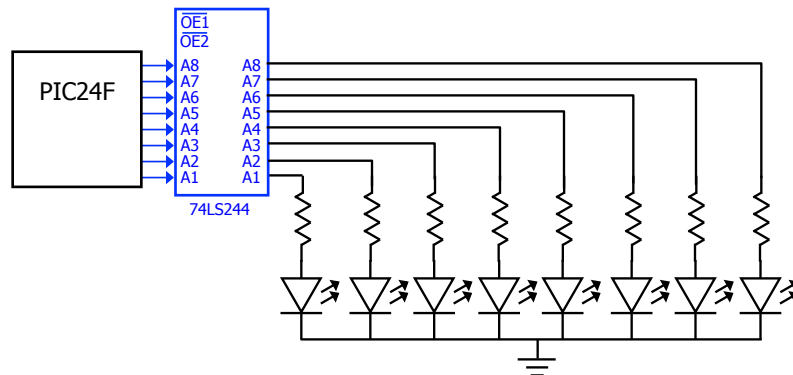
### Digital IO Ports


- Directly Controlling LEDs
  - Limitation - Can only drive as many LEDs as available pins
  - Solutions:
    - Latching
    - Scanning
    - Multiplexing



## ECE 372 – Microcontroller Design
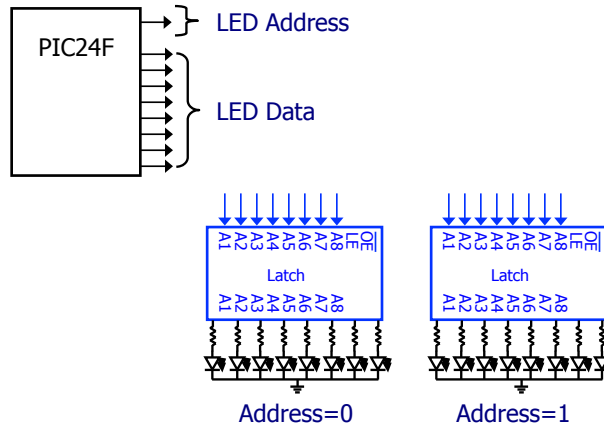
### Digital IO Ports


- LEDs - Latching
  - Control LED by using a latch hardware
  - Use additional hardware to control when to latch values
    - Similar to memory mapped IO



## ECE 372 – Microcontroller Design
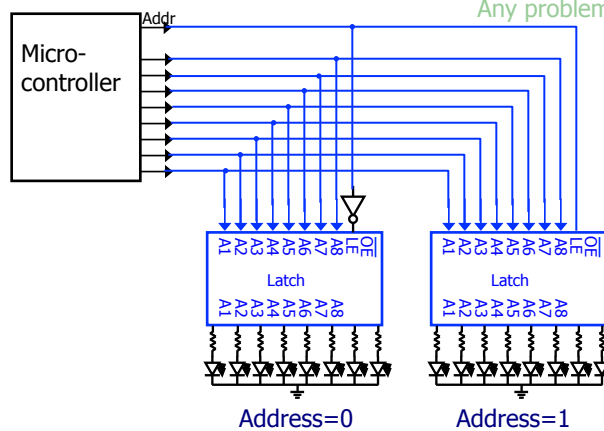
### Digital IO Ports

- LEDs - Latching
  - Control LED by using a latch hardware
  - Use additional hardware to control when to latch values
    - Similar to memory mapped IO




## ECE 372 – Microcontroller Design
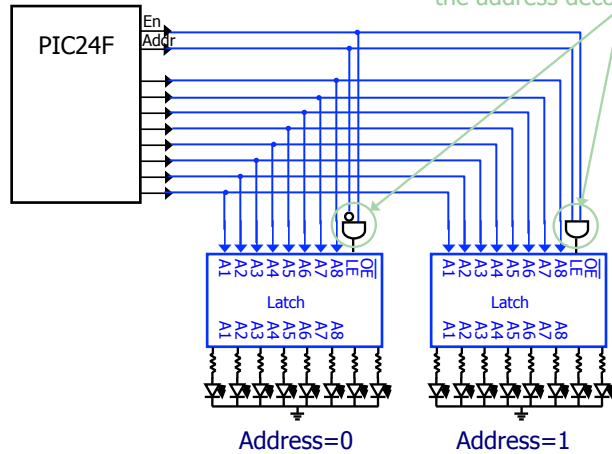
### Digital IO Ports

- LEDs - Latching
  - Add enable signal from microcontroller



What did we build?  
Is there another way to implement the address decoding?



## ECE 372 – Microcontroller Design
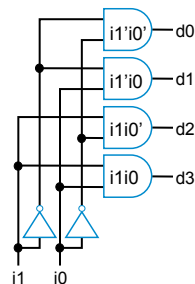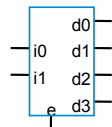
### Digital IO Ports


- LEDs - Latching
  - Use decoder for addressing LED banks
- Decoder - Converts input binary number to *single* high output
  - 2-input decoder: four possible input binary numbers
    - Thus, four outputs, one for each possible input binary number
  - Enable signal
    - Outputs all 0 if e=0
    - Regular behavior if e=1



## ECE 372 – Microcontroller Design
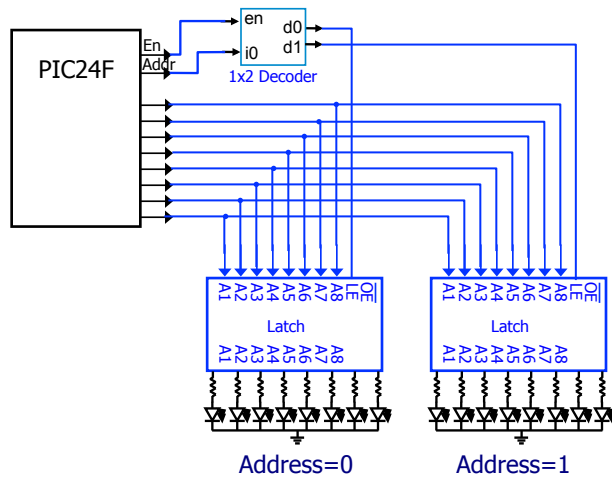
### Digital IO Ports

- LEDs - Latching
  - Use decoder for addressing LED banks



## ECE 372 – Microcontroller Design


### Digital IO Ports

- LEDs - Scanning
  - Use software executing on the microcontroller to control LEDs row by row, col by col, or bank by bank (depending on organization)
  - Operation
    - Continually scan LEDs fast enough that human eye cannot detect it
      - Similar to refresh rate of TVs and Monitors
    - Enable one column of LEDs by writing 0 to output port controlling desired column
    - Write LEDs value for select row
- LEDs – Multiplexed
  - Similar to scanning but uses decoders to specify the row and columns
    - Continually scan LEDs fast enough that human eye cannot detect it
      - Similar to refresh rate of TVs and Monitors
    - Enable LED column by outputting column address to column decoder
    - Enable individual LEDs by outputting row address to row decoder
  - Cannot access all LEDs simultaneously



- Mill Game

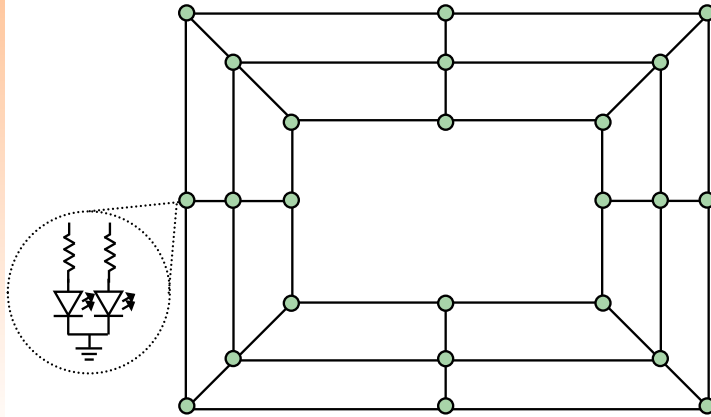
- How many pins do we need to connect the 48 LEDs in the following diagram?



## ECE 372 – Microcontroller Design

Digital IO Ports

- Mill Game

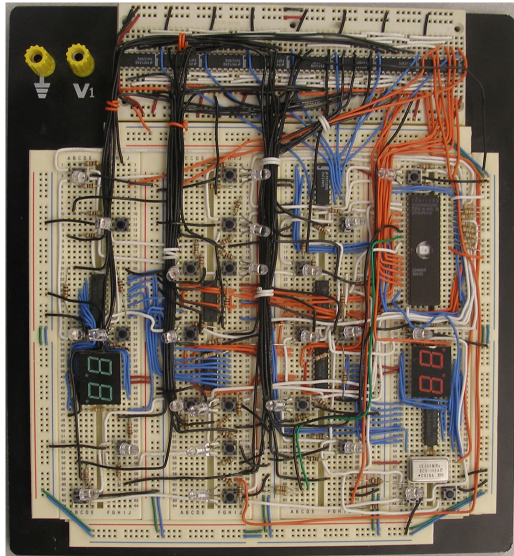


## ECE 372 – Microcontroller Design

Digital IO Ports
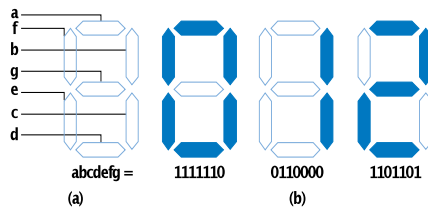
### ○ 7-Segment LEDs

- Can directly control all seven segments using PIC IOs
- Or, driver IC can be used to control display using fewer pins
  - 4 pins instead of 7pins
  - Typically uses BCD to represent displayed value



## ECE 372 – Microcontroller Design

Digital IO Ports

### ○ Keypads


- Collection of several keys grouped into a single device
  - Can buy keypads in many different configurations
  - Build your own keypad using individual buttons
- How can we read dozens of keys on the keypad without requiring dozens on individual input ports on our microprocessor?
  - *Hint: It's similar to how we can interface with dozens of outputs using only a few pins*



## ECE 372 – Microcontroller Design
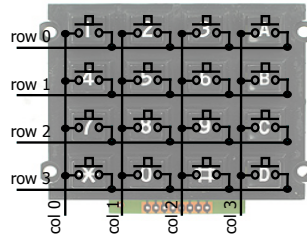
### Digital IO Ports


- Keypad Scanning
  - Similar to scanning for controlling multiple output LEDs
  - Scan the keys one row at a time and read the column lines to see if any key on that row were pressed



## ECE 372 – Microcontroller Design
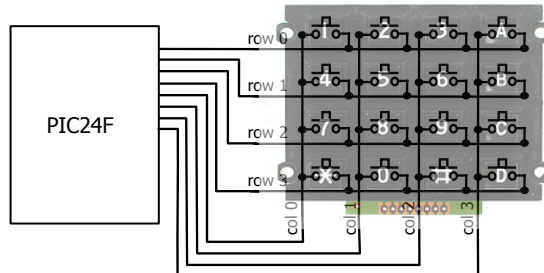
### Digital IO Ports

- Keypad Scanning
  - Similar to scanning for controlling multiple output LEDs
  - Scan the keys one row at a time and read the column lines to see if any key on that row were pressed






## ECE 372 – Microcontroller Design
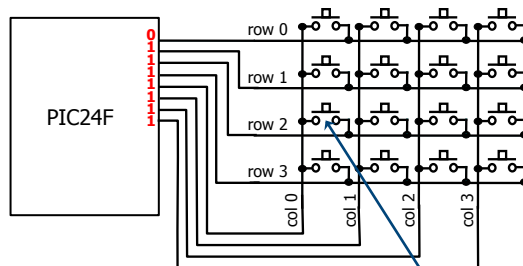
### Digital IO Ports

- Keypad Scanning
  - Similar to scanning for controlling multiple output LEDs
  - Scan the keys one row at a time and read the column lines to see if any key on that row were pressed



1. Set each row output sequentially to output 0


2. Check column inputs to see if key was pressed

What if this key is pressed?

## ECE 372 – Microcontroller Design
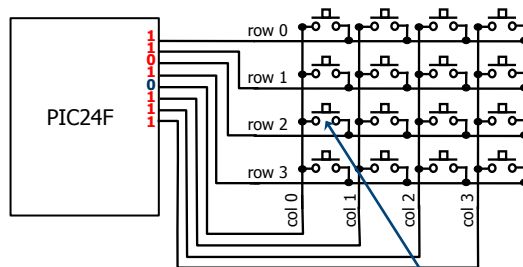
### Digital IO Ports

- Keypad Scanning
  - Similar to scanning for controlling multiple output LEDs
  - Scan the keys one row at a time and read the column lines to see if any key on that row were pressed



1. Set each row output sequentially to output 0


2. Check column inputs to see if key was pressed

What if this key is pressed?

## ECE 372 – Microcontroller Design
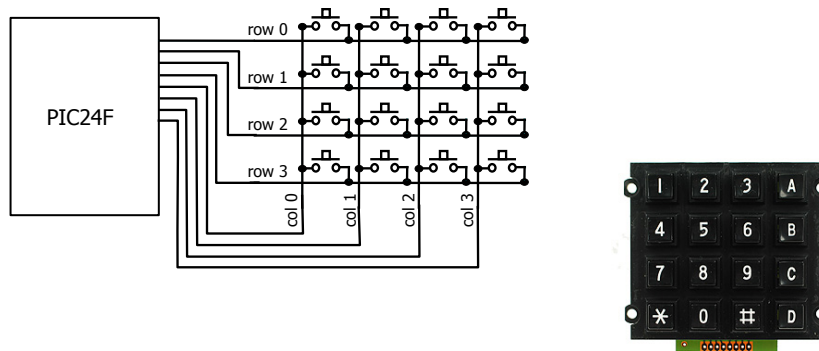
### Digital IO Ports


- Keypad Scanning
  - Can you detect if more than one key is pressed?
  - How do you detect if no keys are pressed?



## ECE 372 – Microcontroller Design

### Digital IO Ports

- Mill Game

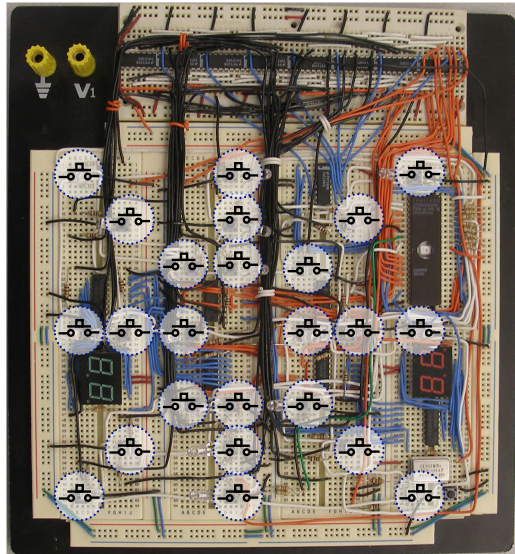

# ECE 372 – Microcontroller Design

Digital IO Ports

- Mill Game

