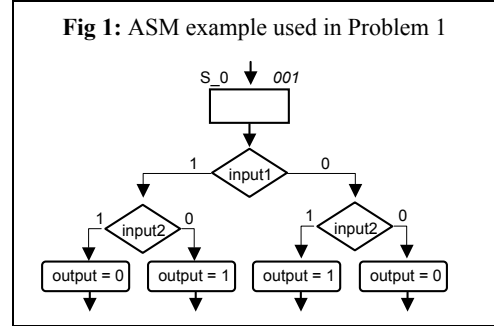


PRACTICE PROBLEM SET 5
ASM Charts and Logic Optimization


- Which function does the ASM in Figure 1 describe?
 - Half Subtractor Borrow Bit
 - 2-to1 MUX
 - Half Subtractor Difference Bit
 - 2-input XOR gate
 - none of the above
- Describe the functionality of a 3-input OR gate using an ASM chart.



- Which of the following equations are in sum-of-minterms form?
 - $F(a, b, c) = 1$
 - $F(a, b, c) = \sum m(1, 2, 3) + \sum d(6)$
 - $F(a, b, c) = ab + a'b'$
 - $F(a, b, c) = abc$
- Implement the following equations using gates (do not optimize the equations). What is the size and area for each circuit?
 - $F = a'$
 - $F = ab + c'$
 - $F = a(b'c' + d) + bd'$
- Plot the following design options on the following graph. Which of the following solutions represent a pareto points?
 - Option A {area = 10, delay = 1 }
 - Option B {area = 2, delay = 2 }
 - Option C {area = 4, delay = 8 }
 - Option D {area = 8, delay = 9 }
 - Option E {area = 1, delay = 8 }
 - Option F {area = 5, delay = 4 }
 - Option G {area = 1, delay = 5 }
 - Option H {area = 9, delay = 6 }
- Use DeMorgan's Law to find the inverse of the following equations. Provide you answer in sum-of-products form.
 - $F(a, b, c, d) = a' + b + c'd$
 - $F = a'bc' + ab$
- Given $F(a, b, c) = ab + ac + a'b'c$
 - List the variables in F
 - List the literals in F
 - List the product terms in F
 - List the minterms in F

8. Consider the equation $F(a,b,c, d) = \sum m(4, 5, 7, 12, 14, 15)$. Which of the following product terms are prime implicants of the equation (*Hint: draw a K-map*).
- $a'bc'd'$
 - $ab'c$
 - ad'
 - $bc'd'$
 - There are no prime implicants in this equation.

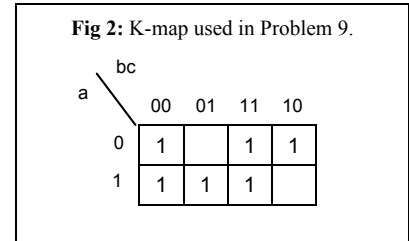9. Using the K-map provided in Fig2, identify
- minterms
 - implicants
 - prime implicants
 - essential prime implicants



10. What is the difference between an exact algorithm and a heuristic?
11. Perform two-level logic optimization for $F(a, b, c, d) = a'b'c'd' + a'c'd' + a'cd' + bed' + acd'$
- Using K-maps, express your solution in sum-of-products form
 - Using Boolean Algebra, express your solution in sum-of-products form
12. Perform two-level logic optimization for $F(a, b, c, d) = \sum(0, 2, 6, 8, 9, 10, 13, 15)$.

13. Using Quine-McCluskey (tabular minimization method) minimize $F(a, b, c) = \sum m(1, 2, 3, 4, 6, 7)$.
14. Using Quine-McCluskey (tabular minimization method) minimize $F(a, b, c) = \sum m(0, 2, 3, 4, 5, 7)$.

Fig 3: Prime Implicants Chart used in Problem 15.

			2	3	7	10	14	15
P_1	001-	(2, 3)	x	x				
P_2	-010	(2, 10)	x			x		
P_3	0-11	(3, 7)		x	x			
P_4	-111	(7, 15)			x			x
P_5	1-10	(10, 14)				x	x	
P_6	111-	(14, 15)					x	x

15. Using Petrick's method, determine the minimum cover of the following prime implicants chart.
16. Petrick's method utilizes the absorption property ($X + XY = X$) to determine the minimum cover. Prove the absorption property works (*NOTE: THIS DOES NOT NEED TO BE A FORMAL PROOF*).
17. How could you change Petrick's method if the size of the prime implicants was taken into consideration (i.e. Size of $a'b'c'$ is 6 transistors vs. ab is only 4 transistors).